

- Announcements
  - Online HW6 due next Monday. No written.
  - This week, Ch. 9/10
- Last Time
  - Circuits, current, voltage, charge
  - Series/parallel resistors/capacitors
  - Kirchoff's "laws"
- Today
  - Internal resistance
  - EMF
  - Resistance and resistivity

Scientists:

What's true? Are there exceptions?

How does it work?

Why does it work?

How does it relate to things we already knew?

How can I make it simple?

## Scientists:

What's true? Are there exceptions?

How does it work?

Why does it work?

How does it relate to things we already knew?

How can I make it simple?

## Engineers:

It's true most of the time, good enough!

That's cool!

What can I build with it?

Oh ... by the way, why doesn't my thing work right?

Power is the product  
of voltage and current  
(True for ALL devices)

$$P = IV$$

Ohm's law (resistors only)

$$V = IR$$

Resistor power  
dissipation

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

Resistance in terms of  
Resistivity

$$R = \rho \frac{L}{A} = \frac{L}{\sigma A}$$

Current density

$$I = \vec{J} \cdot \vec{A} \quad \vec{J} = \sigma \vec{E}$$


Drude Model

$$\vec{J} = n q \vec{v}_{\text{drift}}$$

- **EMF and Voltage**
- How Kirchoff's Rules lead to parallel/series formulae
- Internal Resistance
- Resistance and Resistivity
- Drude Model of Conduction
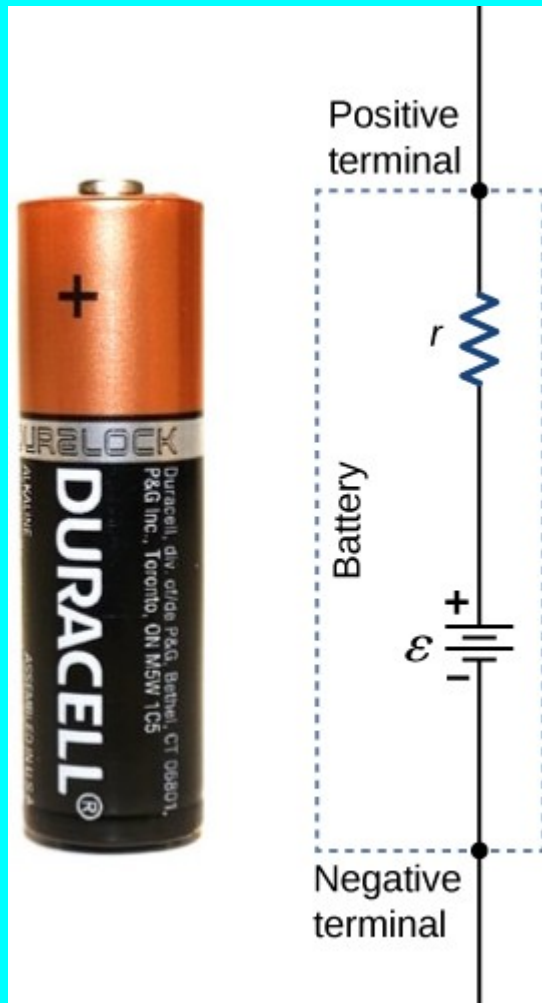
# EMF vs. Voltage

When the current inside flows **AGAINST** the electric field (e.g. a battery) we call it **EMF**.



# EMF vs. Voltage

When the current inside flows **AGAINST** the electric field (e.g. a battery) we call it EMF.

To make it less confusing ... haha

It is fine to consider that voltage and EMF are the same thing.

Just call everything “voltage”





- EMF and Voltage
- How Kirchoff's Rules lead to parallel/series formulae
- Internal Resistance
- Resistance and Resistivity
- Drude Model of Conduction

# Kirchoff's "Laws"

## Voltage Law

In a series circuit, voltages across the parts add up to the Battery voltage

## Current Law

In a parallel circuit, currents across the parts add up to the battery current. (In a series circuit all currents are the same)

# Resistors and Capacitors in Series & Parallel

$$V = \frac{Q}{C}$$

$$\frac{1}{C_{\text{series}}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots$$

$$V = IR$$

$$R_{\text{series}} = R_1 + R_2 + R_3 + \dots$$

$$C_{\text{parallel.}} = C_1 + C_2 + C_3 + \dots$$

$$\frac{1}{R_{\text{parallel.}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Resistors (and capacitors) in parallel have equal voltages.



Resistors (and capacitors) in series have equal currents.



# Series circuits:


Same current in every part of circuit

Voltage drops at every resistor

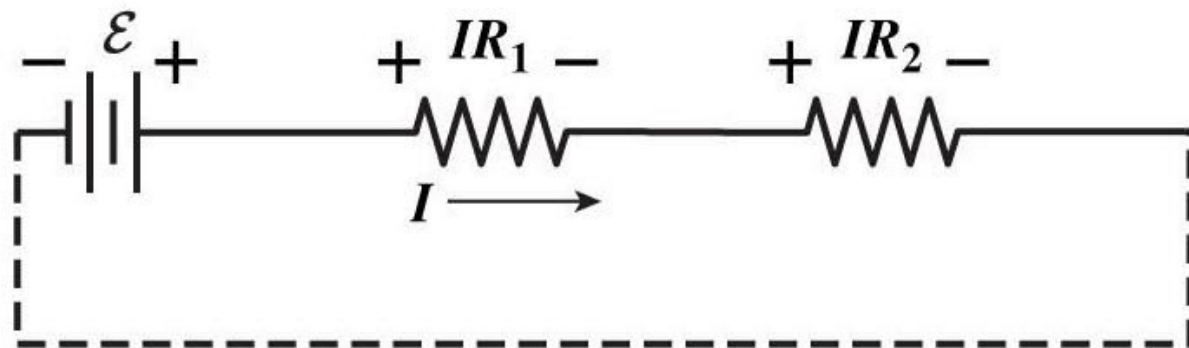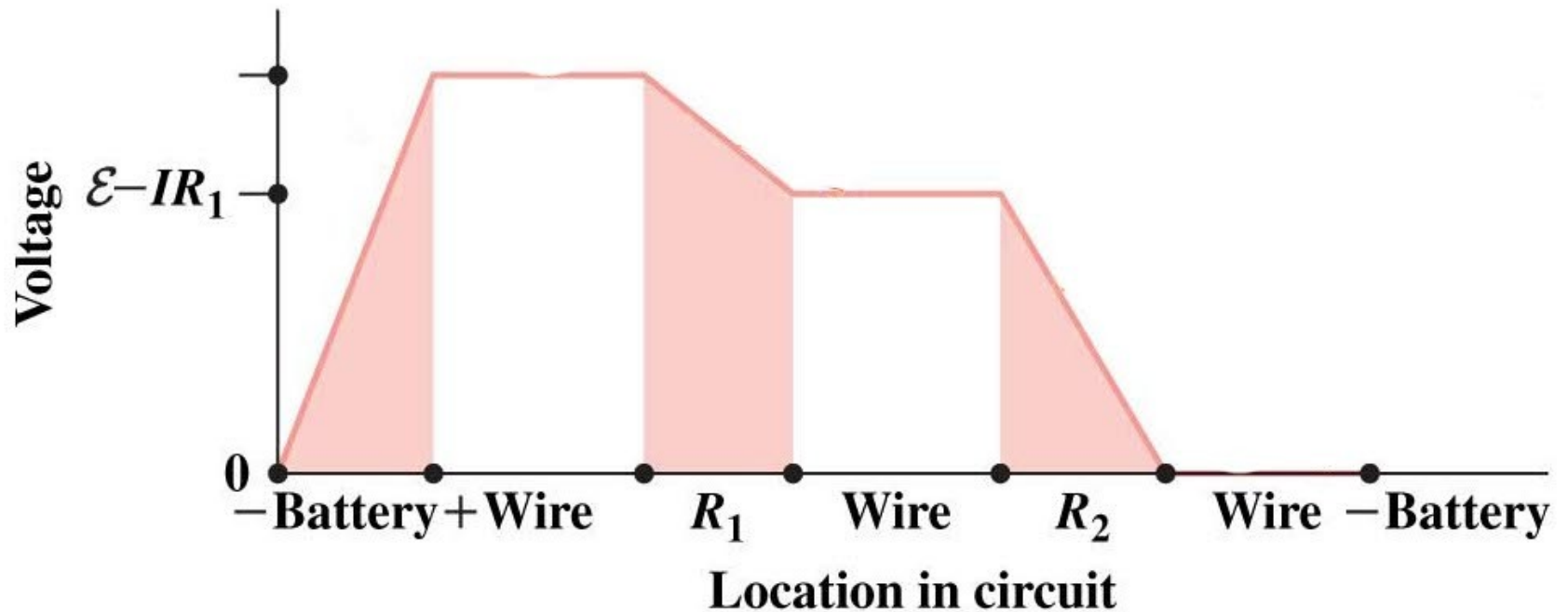


# Series circuits:

All light bulbs equally bright ...

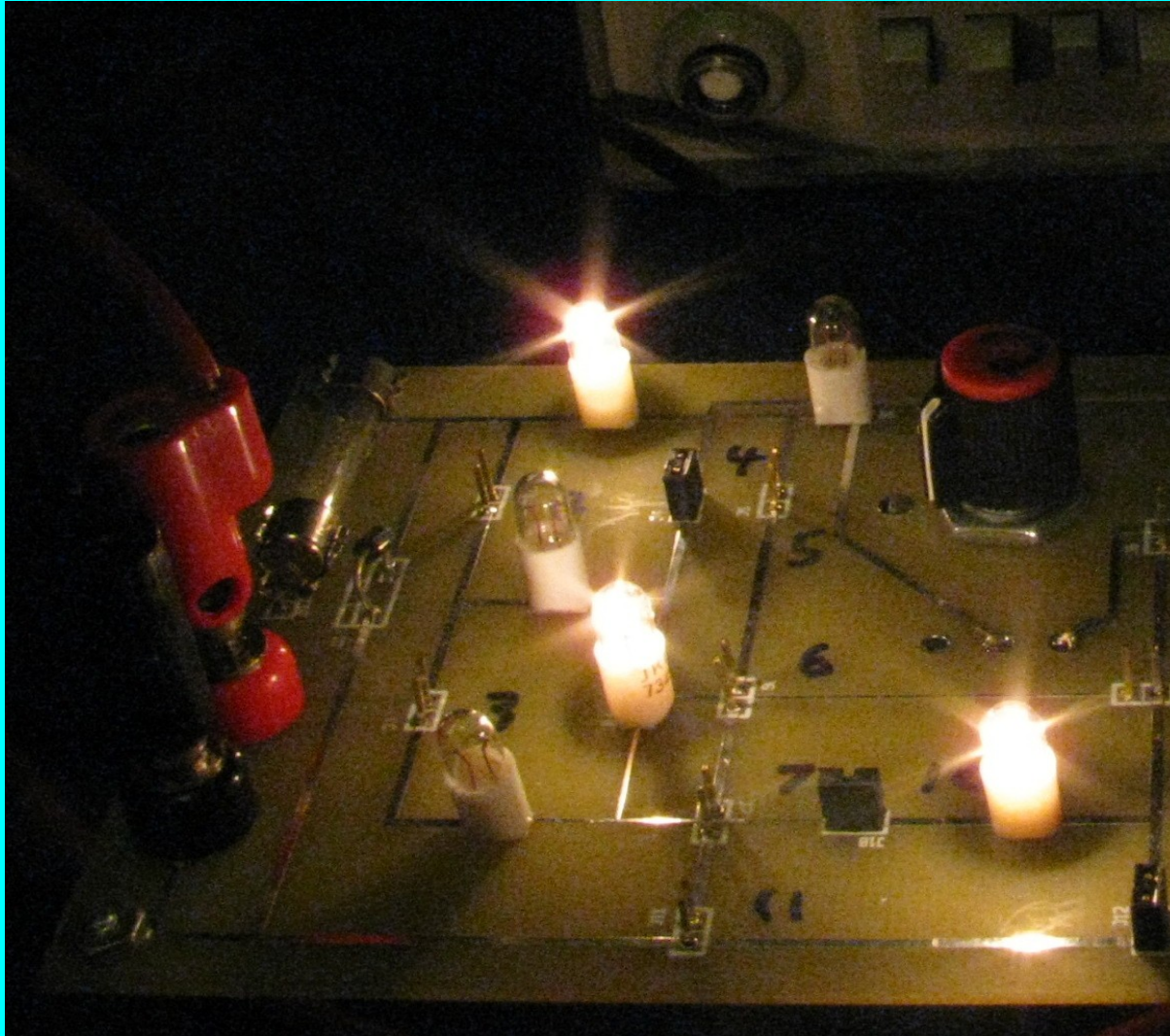
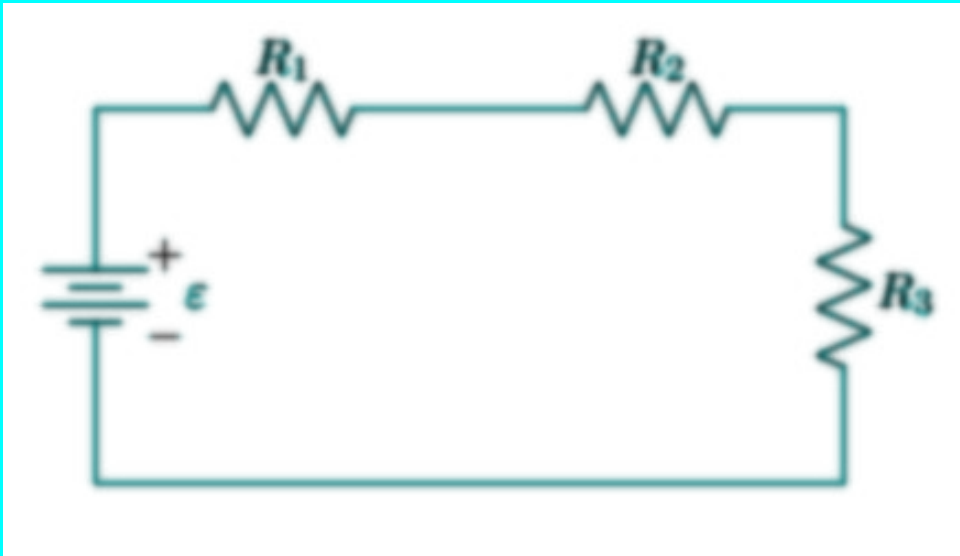
# Origin of series formula

$$R_{\text{equivalent}} = R_1 + R_2 + R_3 + \dots$$








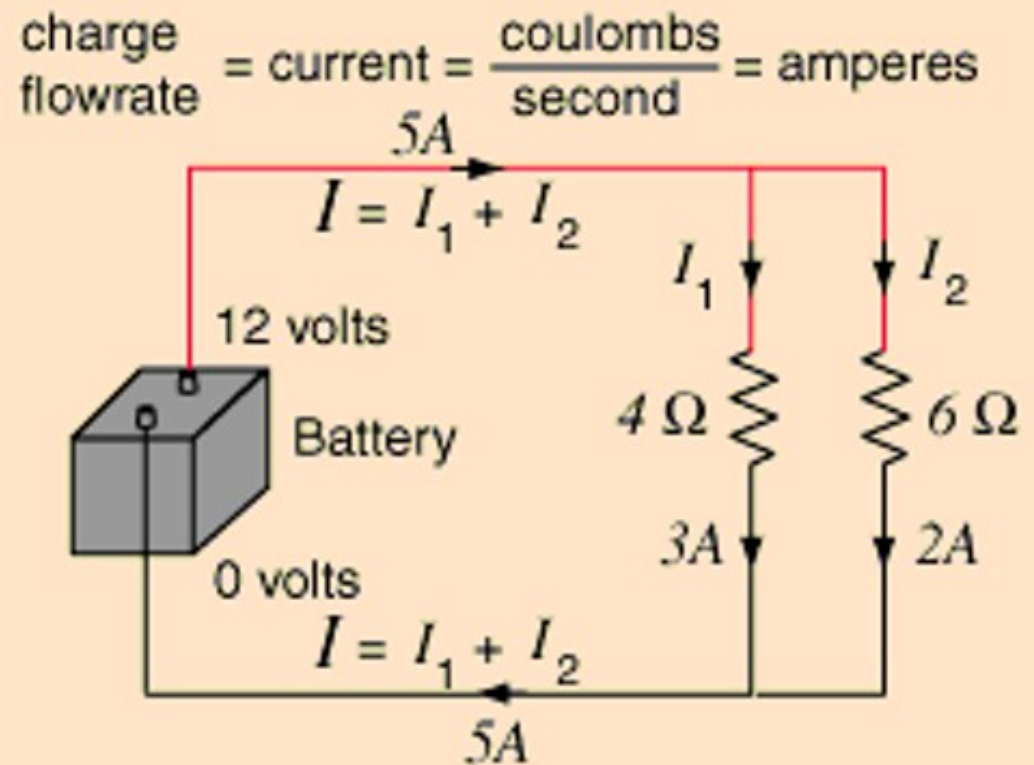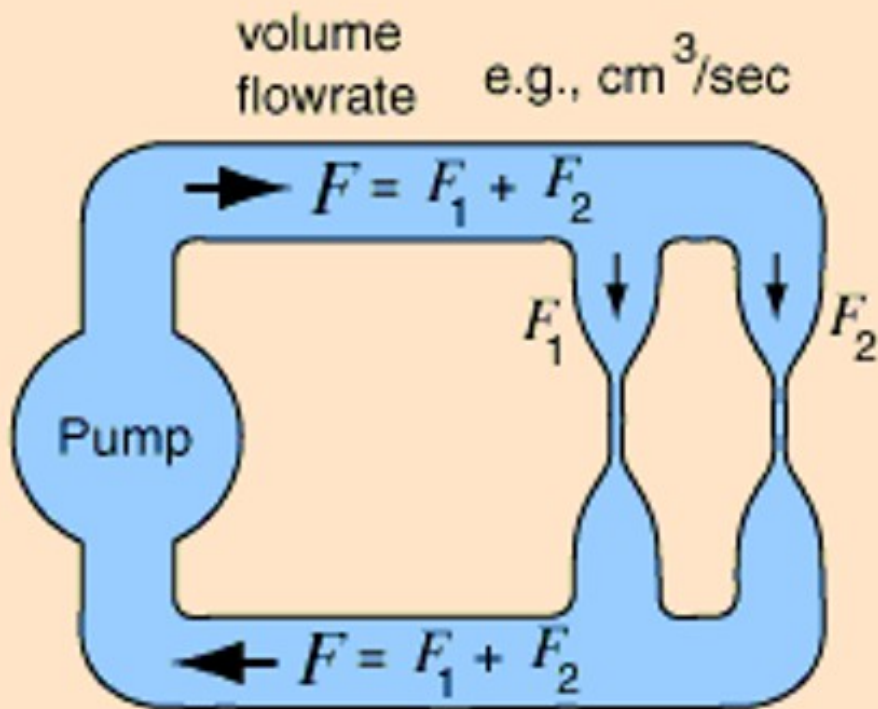
# Parallel circuits:


Same voltage drop across resistors.  
Current splits between resistors.

$$\frac{1}{R_{\text{equivalent}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



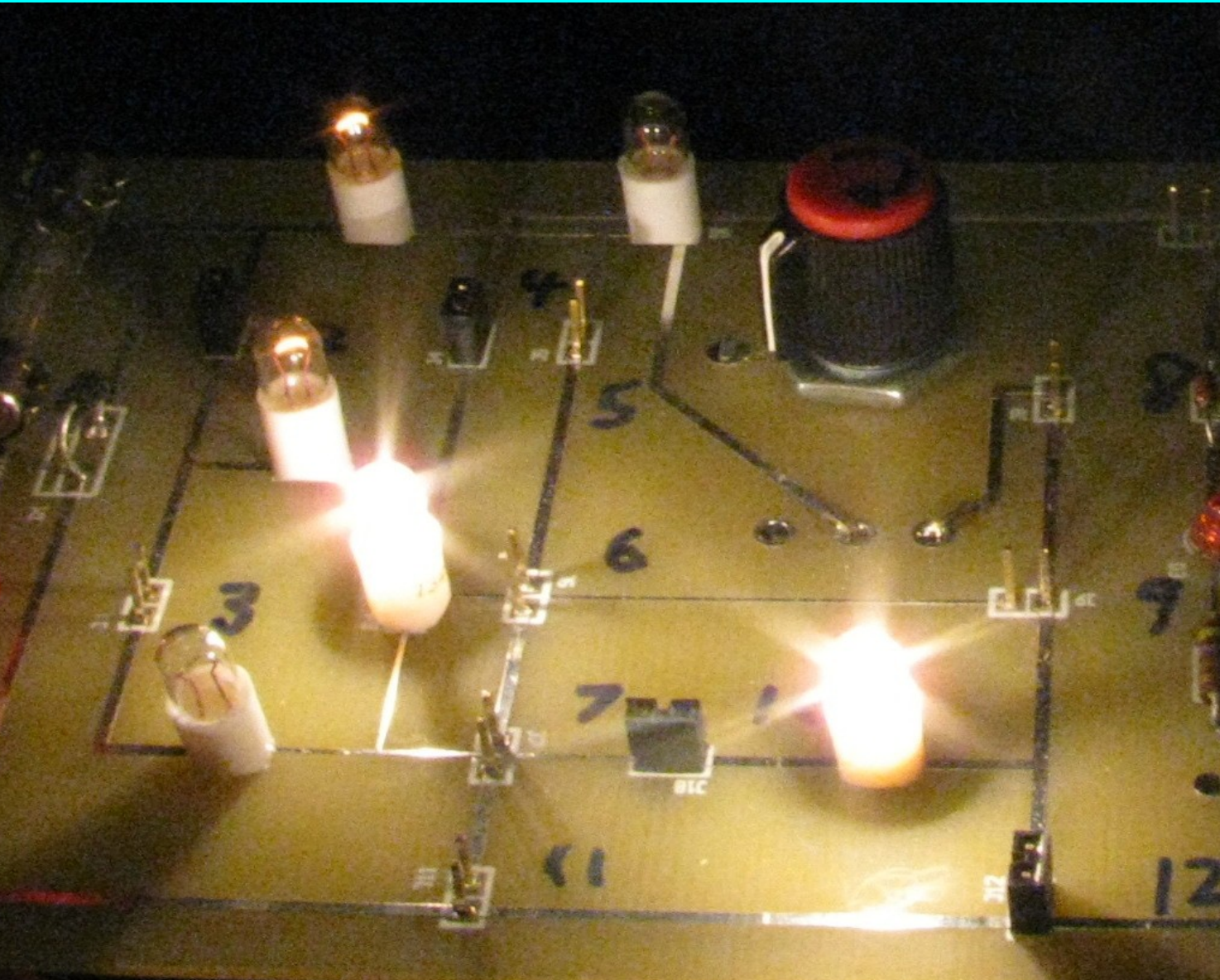
# Parallel circuits:


Same voltage drop across resistors.  
Current splits between resistors.


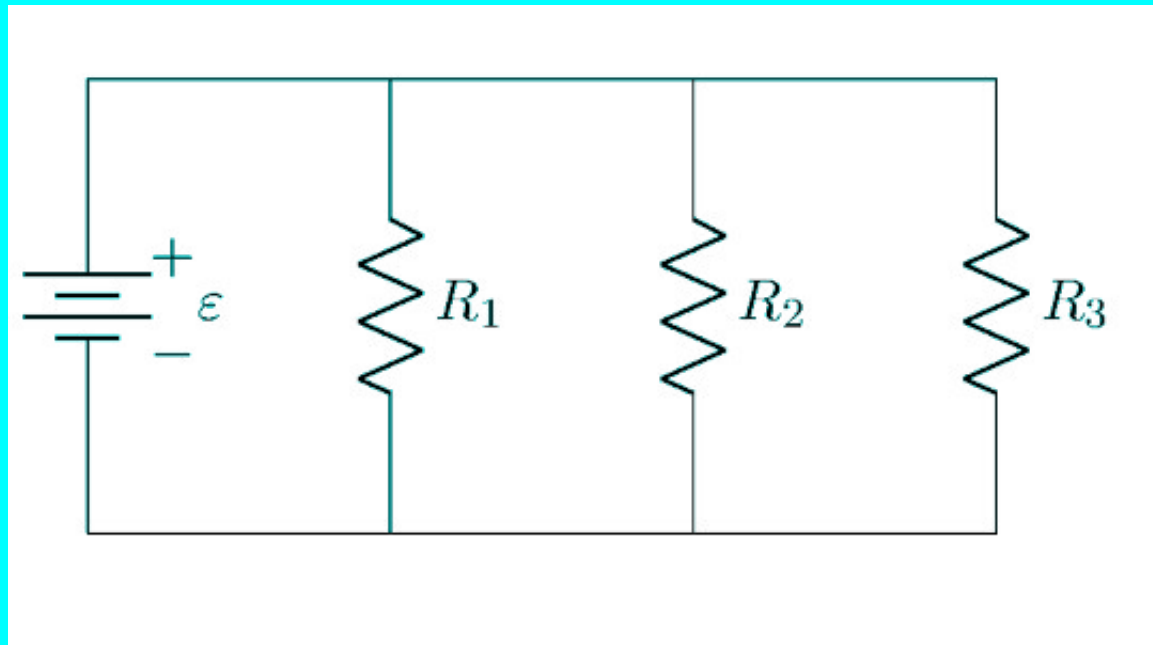
# Origin of parallel formula


$$\frac{1}{R_{\text{equivalent}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$



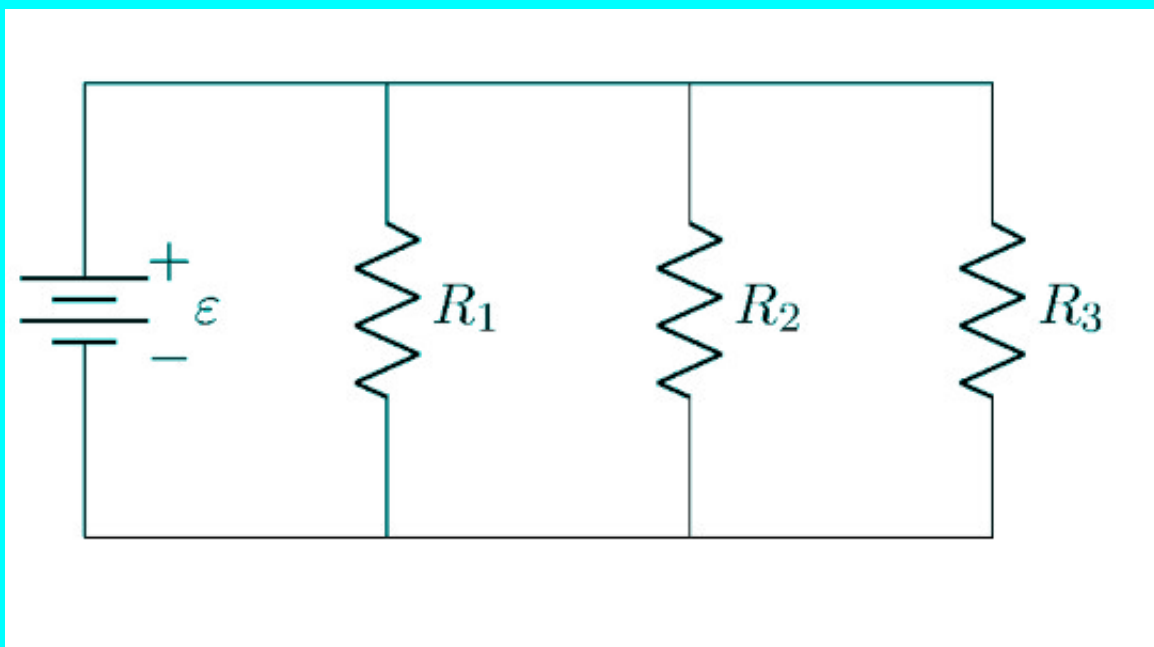

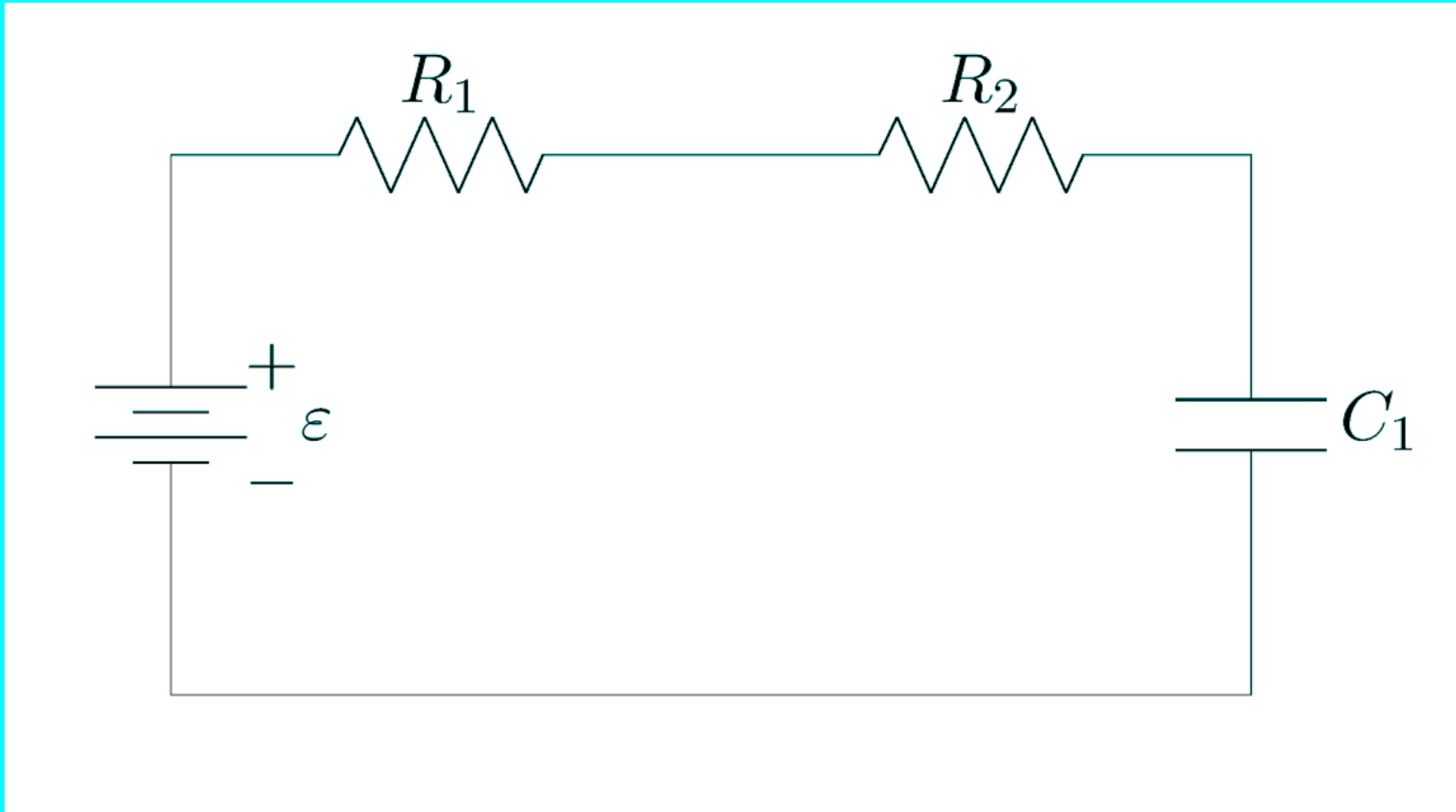
# What is the voltage across $C_1$ ?

$$\varepsilon = 10 \text{ V}; I_1 = 2 \text{ A}; R_1 = 1 \Omega, R_2 = 2 \Omega$$


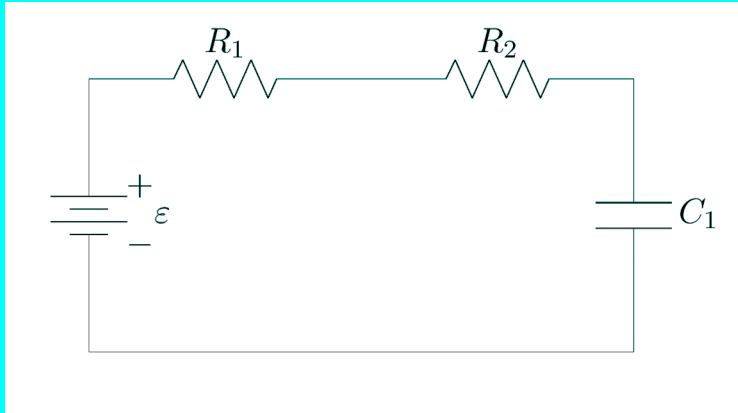
# What is the voltage across $C_1$ ?

$$\varepsilon = 10 \text{ V}; I_1 = 2 \text{ A}; R_1 = 1 \Omega, R_2 = 2 \Omega$$



**(A)**  $1 \text{ V}$

**(D)**  $6 \text{ V}$

**(B)**  $2 \text{ V}$

**(E)**  $10 \text{ V}$


**(C)**  $4 \text{ V}$


- EMF and Voltage
- How Kirchoff's Rules lead to parallel/series formulae
- **Internal Resistance**
- Resistance and Resistivity
- Drude Model of Conduction

# Internal Resistance

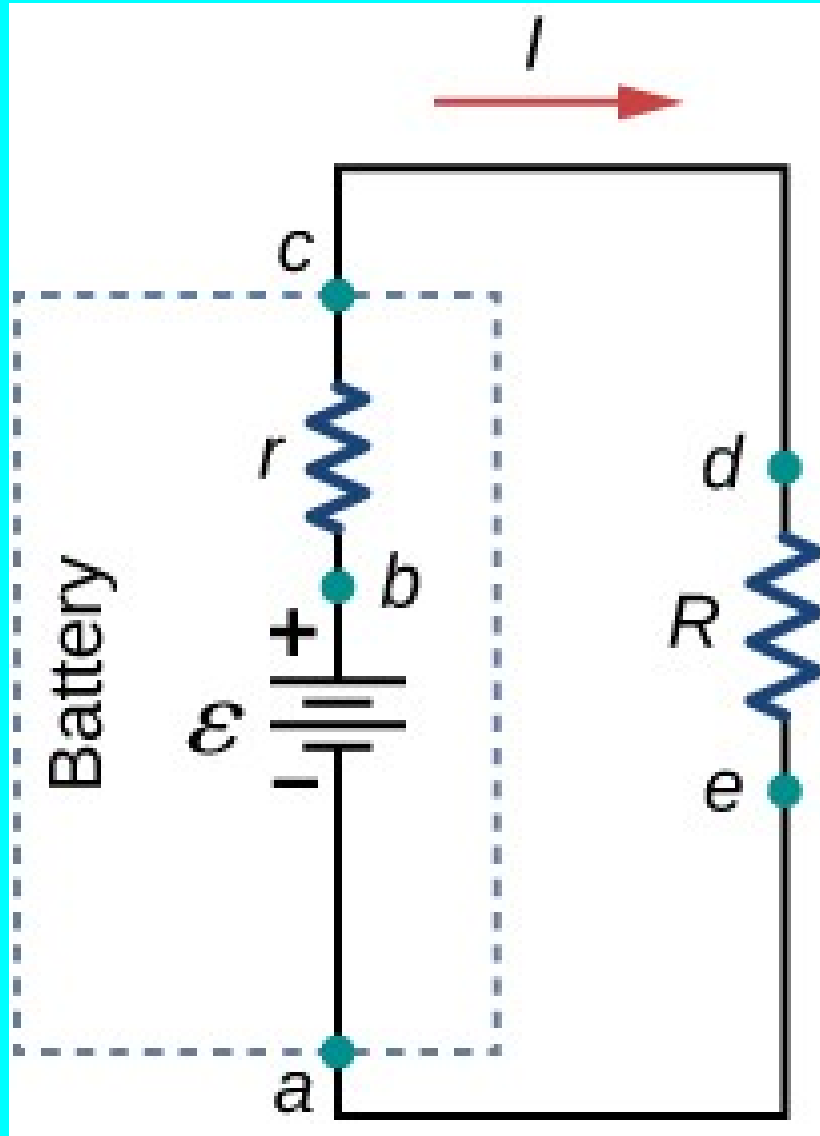**Why can't you start a car with AA batteries?**





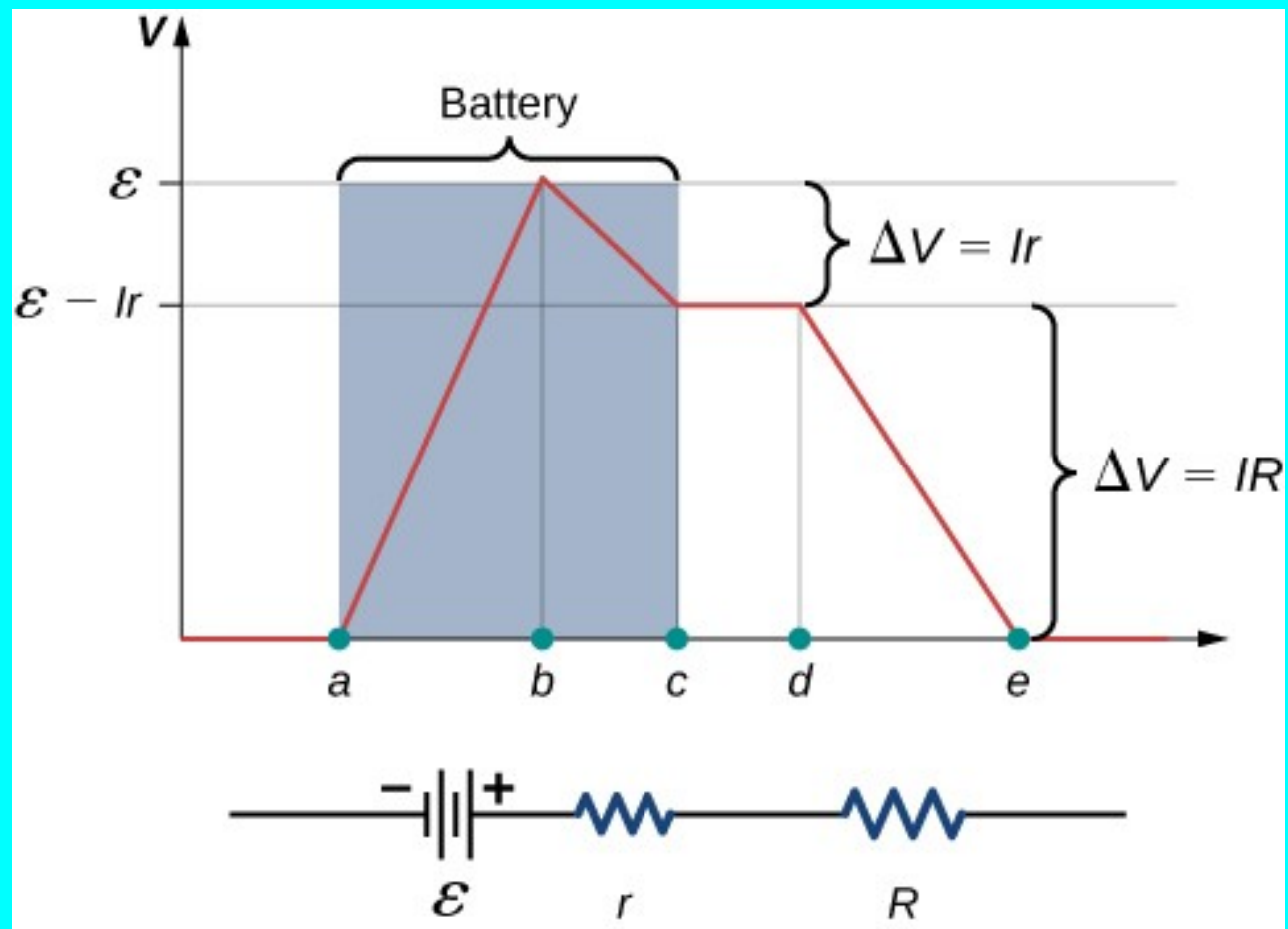

**A 12 Volt car battery has 0.01 Ohm internal resistance**

The Engine takes 500 Amps to start.

What voltage do you measure at the battery terminals?

**(A) 1 V**

**(D) 7 V**

**(B) 3 V**

**(E) 12 V**

**(C) 5 V**

# Internal Resistance

**Why can't you start a car with AA batteries?**

**Clickers:** A  $2.0\ \Omega$  resistor is in series with a  $6.0\ \Omega$  resistor. If the  $2.0\ \Omega$  resistor has a current of  $1.0$  Amp, what is the current through the  $6.0\ \Omega$  resistor?

[A] also  $1.0$  Amp


[B]  $0.333$  Amp

[C]  $6.0$  Amps


[D]  $3.0$  Amps

[E] Need more information to decide.

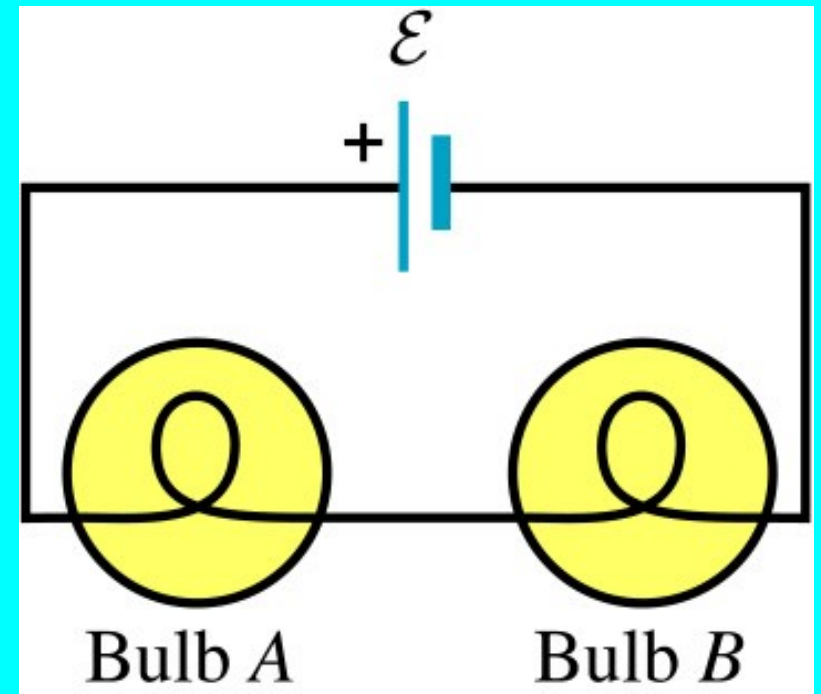In the circuit shown, the two bulbs  $A$  and  $B$  are identical. Compared to bulb  $A$ ,



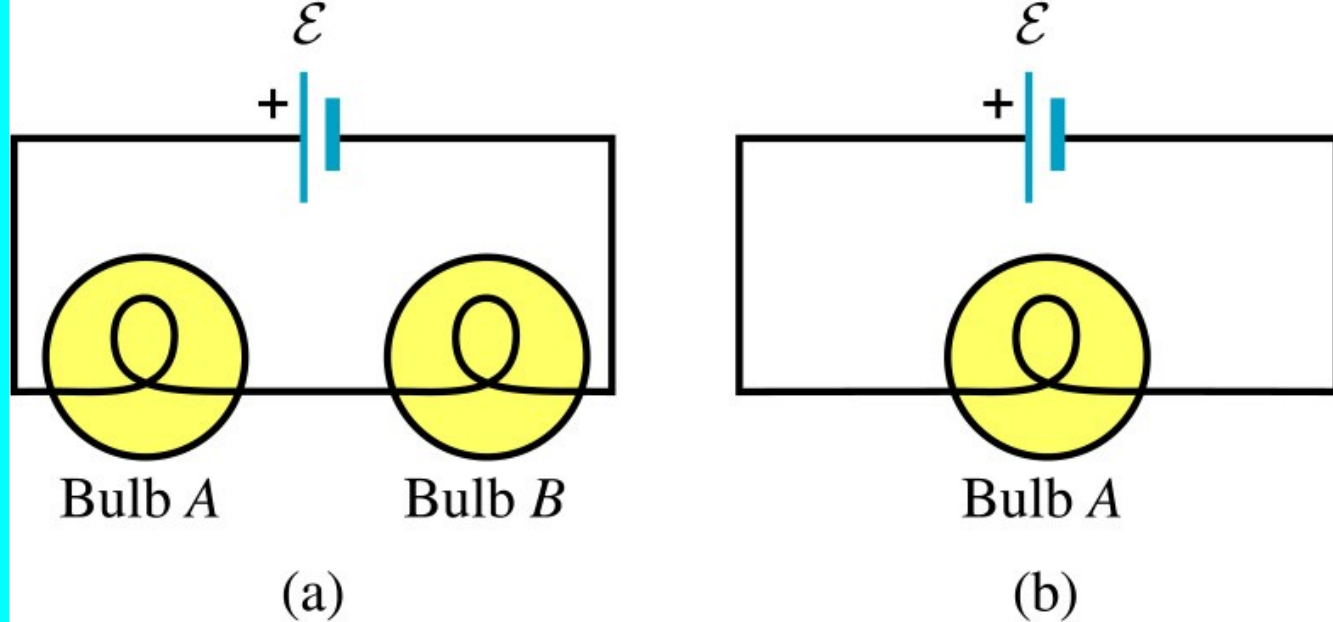- A. bulb  $B$  glows more brightly
- B. bulb  $B$  glows less brightly
- C. bulb  $B$  glows just as brightly
- D. answer depends on whether the mobile charges in the wires are positively or negatively charged



In the circuit shown in (a), the two bulbs *A* and *B* are identical. Bulb *B* is removed and the circuit is completed as shown in (b). Compared to the brightness of bulb *A* in (a), bulb *A* in (b) is

- A. brighter
- B. less bright
- C. just as bright
- D. any of the above





- EMF and Voltage
- How Kirchoff's Rules lead to parallel/series formulae
- Internal Resistance
- Resistance and Resistivity
- Drude Model of Conduction

Power is the product  
of voltage and current  
(True for ALL devices)

$$P = IV$$

Ohm's law (resistors only)

$$V = IR$$

Resistor power  
dissipation

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

Resistance in terms of  
Resistivity


$$R = \rho \frac{L}{A} = \frac{L}{\sigma A}$$


Current density


$$I = \vec{J} \cdot \vec{A} \quad \vec{J} = \sigma \vec{E}$$

Drude Model


$$\vec{J} = n q \vec{v}_{\text{drift}}$$

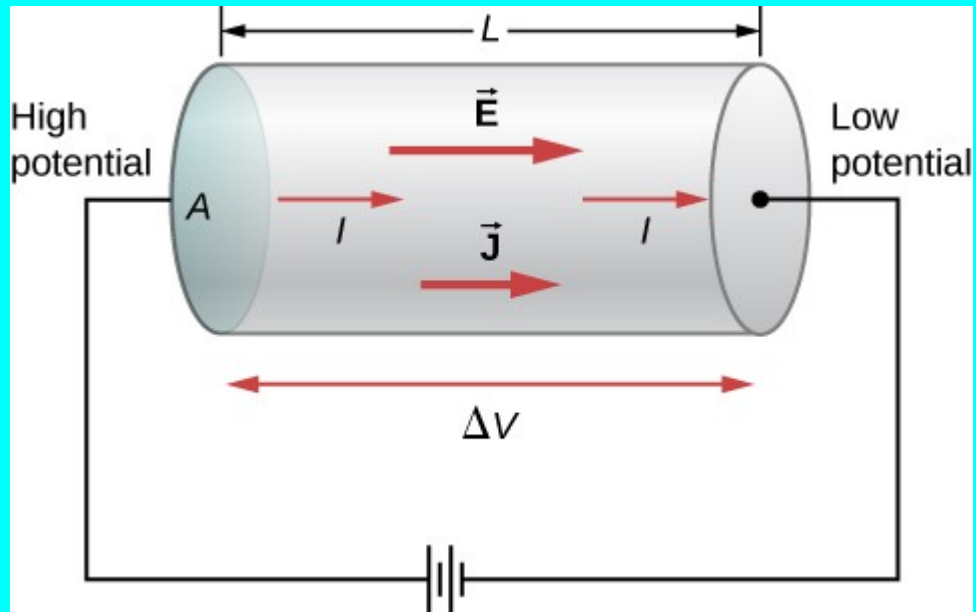

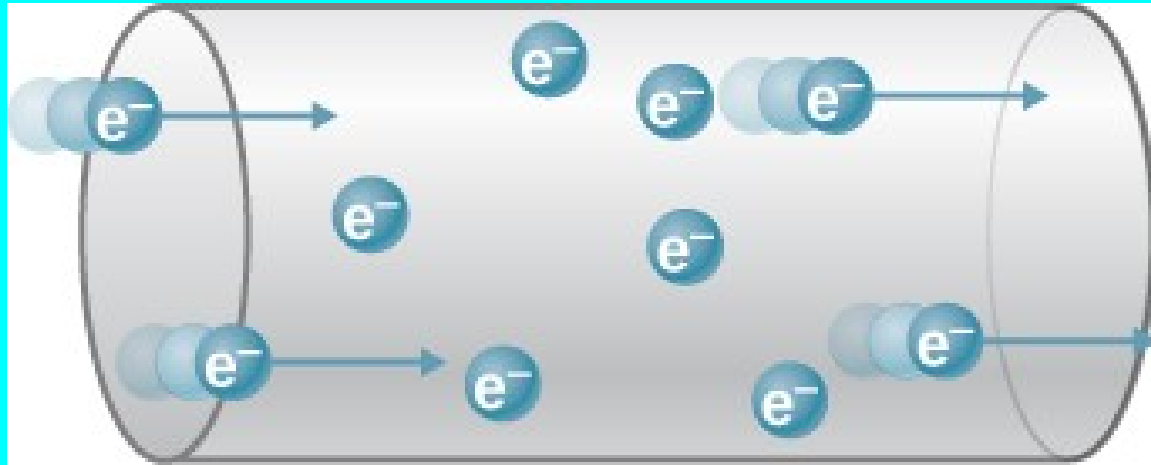

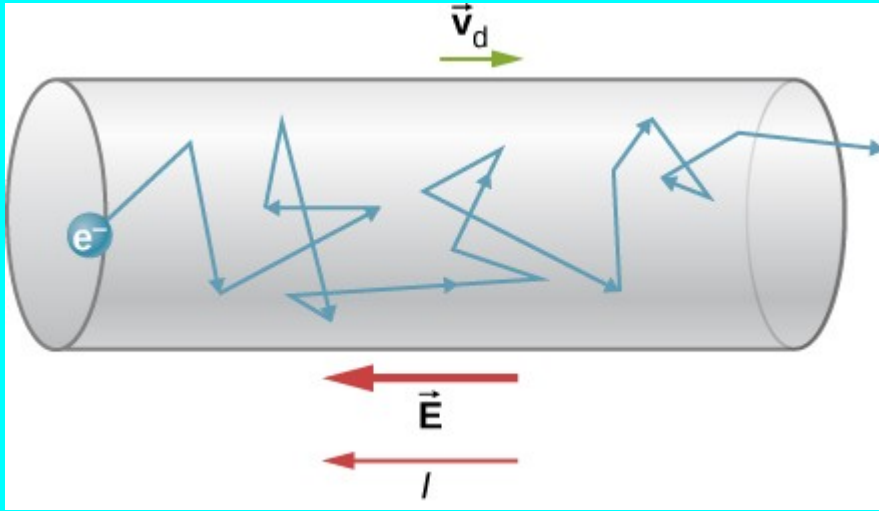




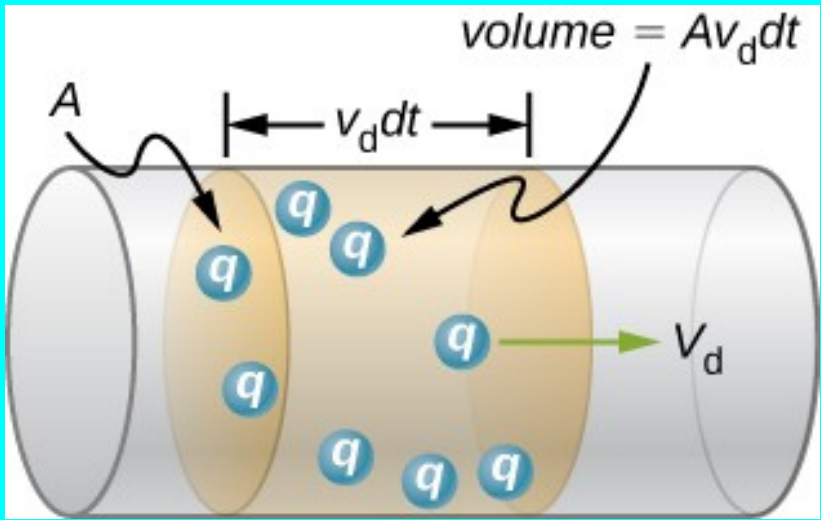





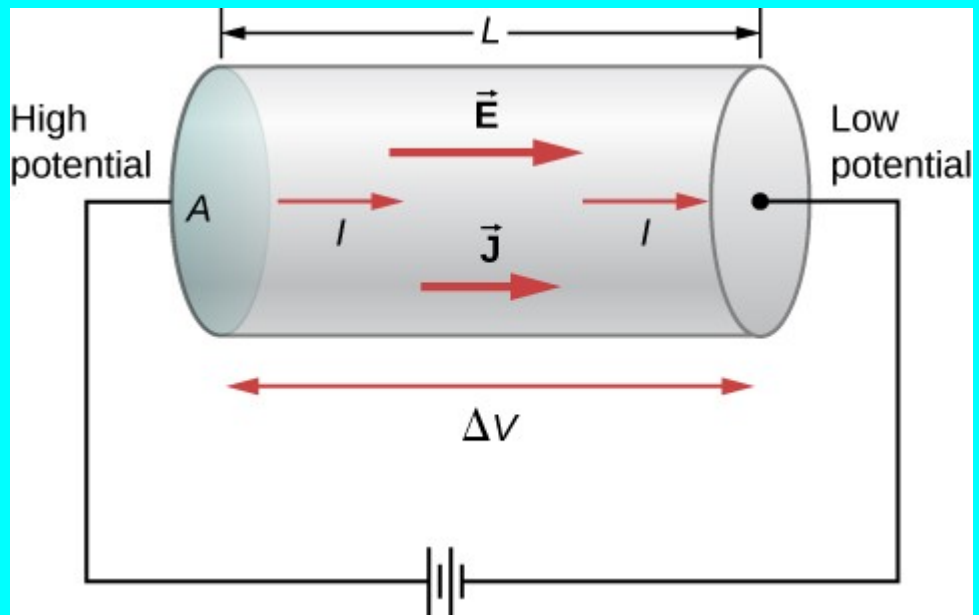

# Circuit Simulator

[https://phet.colorado.edu/sims/html/circuit-construction-kit-dc/latest/circuit-construction-kit-dc\\_all.html](https://phet.colorado.edu/sims/html/circuit-construction-kit-dc/latest/circuit-construction-kit-dc_all.html)

# LECTURE 18 RECAP

- EMF and Voltage
- How Kirchoff's Rules lead to parallel/series formulae
- Internal Resistance
- Resistance and Resistivity
- Drude Model of Conduction

## Scientists:

What's true? Are there exceptions?

How does it work?

Why does it work?

How does it relate to things we already knew?

How can I make it simple?

## Engineers:

It's true most of the time, good enough!

That's cool!

What can I build with it?

Oh ... by the way, why doesn't my thing work right?

# Managers:

How can we make more money?

If we rush the engineers, can we still sell it without getting sued?

Who wants scientists? ... they just want to mess around in the lab all day.

Can't we just hire young engineers? The old ones cost too much and tell us what won't work.