

- Announcements
  - Exam 2 in April 2 (Next Tuesday)
  - Lab next week, electrons in magnetic field
  - Midterm grades – Email me w/ questions
- Last Time
  - Intro to magnetism
- Today
  - Some review
  - Potential
  - Resistance and resistivity
  - Circuit analysis
  - Intro to magnetism

# Problem

- What is the resistance of a piece of wire given the material, length, and diameter?

$$R = \rho \frac{L}{A} = \frac{L}{\sigma A}$$

- How much power does it dissipate?

$$P = IV = I^2 R = \frac{V^2}{R}$$

**Problem 11:** A piece of 14-gauge copper wire has a length of 7.25 m. The tables provided may be a convenient source of data.

Wire diameter  $d$  for select gauges in the AWG (American Wire Gauge) system.

<b>gauge</b>	0	2	4	6	8	10	12	14	16	18	20
<b>d (mm)</b>	8.251	6.544	5.189	4.115	3.264	2.588	2.053	1.628	1.291	1.024	0.812

Conductivity ( $\sigma$ ), resistivity ( $\rho$ ), and temperature coefficient of resistivity ( $\alpha$ ) at 20°C for select materials.

<b>material</b>	$\sigma$ ( $1/(\Omega \cdot \text{m})$ )	$\rho$ ( $\Omega \cdot \text{m}$ )	$\alpha$ ( $^{\circ}\text{C}^{-1}$ )
<b>conductors</b>			
silver	$6.29 \times 10^7$	$1.59 \times 10^{-8}$	$3.8 \times 10^{-3}$
copper	$5.95 \times 10^7$	$1.68 \times 10^{-8}$	$3.9 \times 10^{-3}$
gold	$4.10 \times 10^7$	$2.44 \times 10^{-8}$	$3.4 \times 10^{-3}$
aluminum	$3.77 \times 10^7$	$2.65 \times 10^{-8}$	$3.9 \times 10^{-3}$



# Ampacity Charts | Wire Gauge Chart

## IN THIS SECTION

### Overview

### Tables & Calculators

[Ampacity Calculator](#)

[Ampacity Charts](#) 

[Applications Charts](#)

[Product Applications](#)

[Raceway Fill Calculator](#)

[Voltage Drop Calculator](#)

[Voltage Drop Tables](#)

### Installation Guide

### ReelRover Tools

## Wire Size & Amp Ratings

Wire Gauge Size	Copper			Aluminum	
	60°C (140°F) NM-B, UF-B	75°C (167°F) THW, THWN, SE, USE, XHHW	90°C (194°F) THWN-2, THHN, XHHW-2, USE-2	75°C (167°F) THW, THWN, SE, USE, XHHW	90°C (194°F) XHHW-2, THHN, THWN-2
14	15	20	25	---	---
12	20	25	30	20	25
10	30	35	40	30	35
8	40	50	55	40	45
6	55	65	75	50	55

# Problem


- An electron begins at 1000 m/s and then crosses a 2000 V potential drop.
- What is its final speed?

$$m_e = 9.11 \times 10^{-31} \text{ kg}$$

$$U = QV$$



# Next Week's Lab

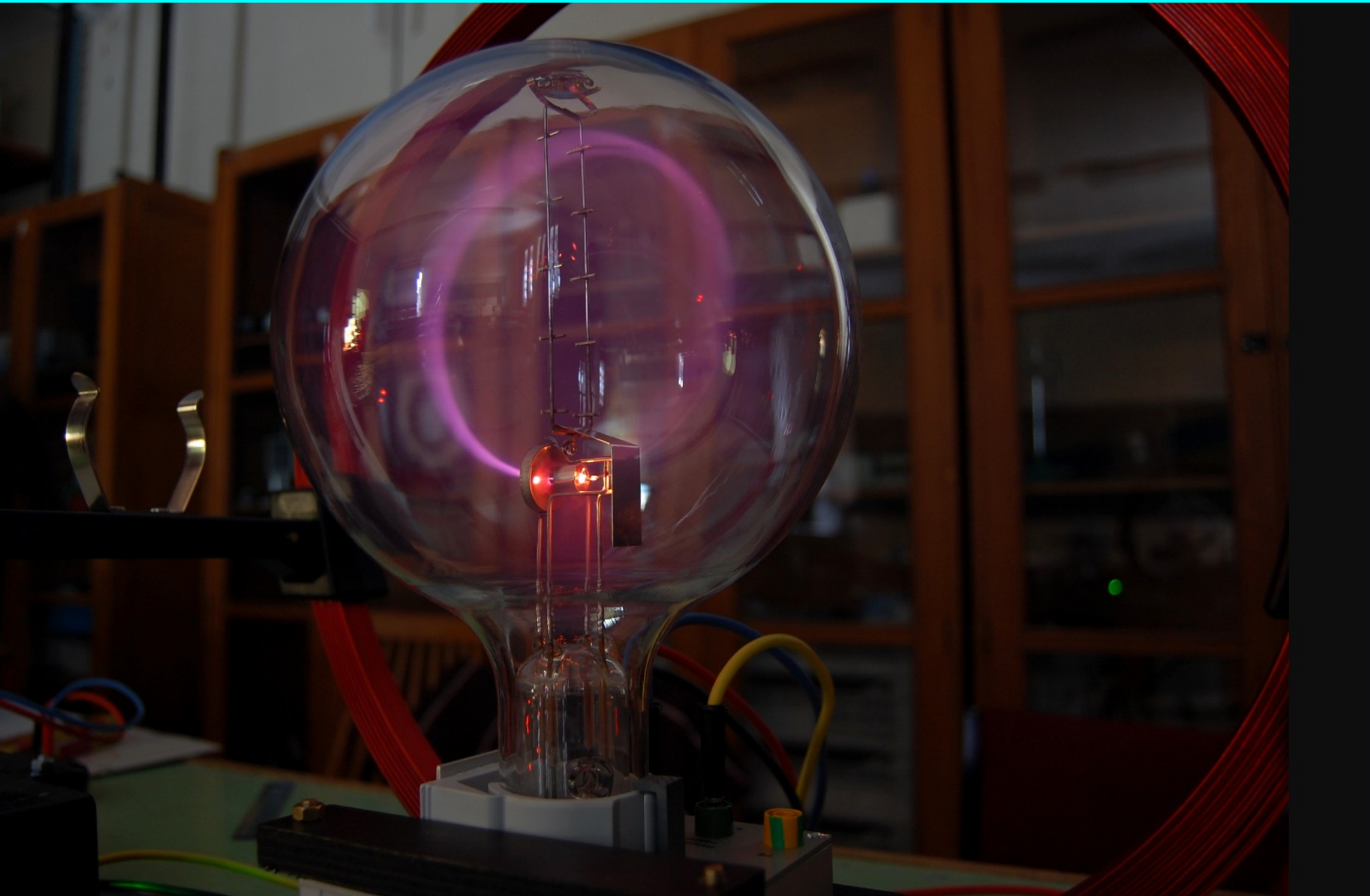




# Problem

- What is the capacitance of the Earth?

$$R_e = 6400 \text{ km}$$

$$Q = CV$$

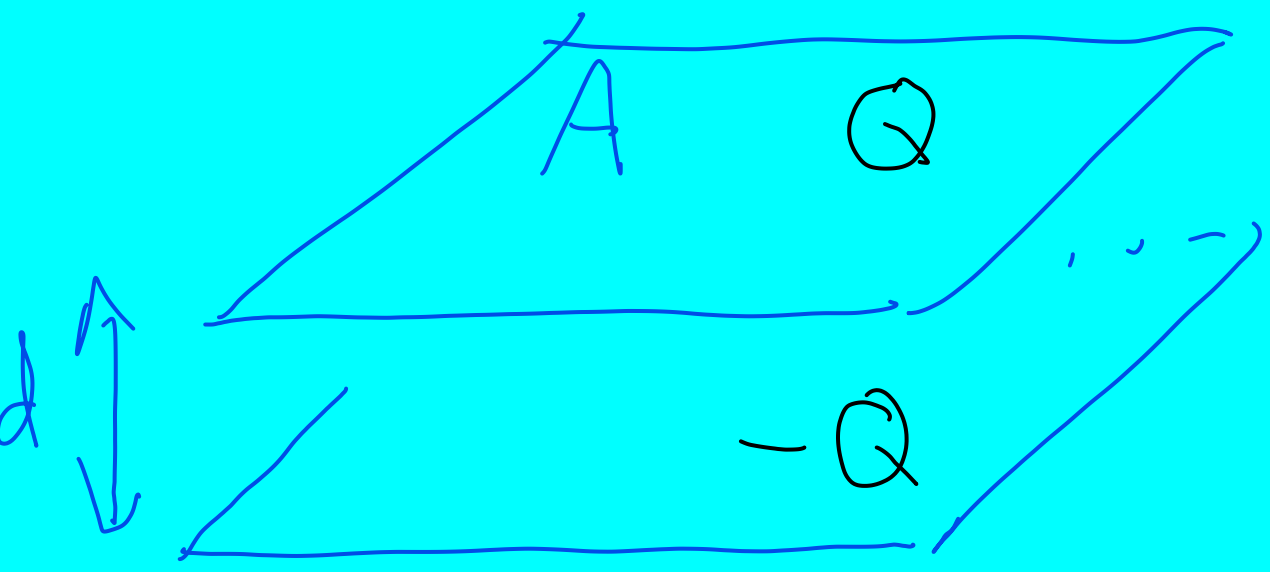

$$\epsilon = \frac{Q}{A\epsilon_0}$$
~~$$\epsilon = \frac{Q}{\epsilon_0}$$~~

$$\underline{Q = CV}$$

$$\epsilon = \frac{Q}{A\epsilon_0}$$

$$V = \epsilon \Delta z$$

$$V = \epsilon d = \frac{Q}{A\epsilon_0} d$$

$$\Delta z = d$$

$$\underline{Q = \frac{A\epsilon_0}{d} V}$$

$$\underline{\underline{E = V/d}}$$

**Problem 3:** Suppose you have a 9.00 V battery, a 2.6  $\mu\text{F}$  capacitor, and a 8.25  $\mu\text{F}$  capacitor.

@theexpertta.com - tracking id: 3N77-CA-1B-47-BD54-51052. In accordance with Expert TA's Terms of Service, copying this information to any solutions sharing website is strictly forbidden. Doing so may result in termination of your Expert TA Account.

**Part (a)** Find the total charge stored in the system if the capacitors are connected to the battery in series in C.

**Numeric** : A numeric value is expected and not an expression.

$Q =$  \_\_\_\_\_

**Part (b)** Find the energy stored in the system if the capacitors are connected to the battery in series in J.

**Numeric** : A numeric value is expected and not an expression.

$U_s =$  \_\_\_\_\_

**Part (c)** Find the charge if the capacitors are connected to the battery in parallel in C.

**Numeric** : A numeric value is expected and not an expression.

$Q =$  \_\_\_\_\_

**Part (d)** Find the energy stored if the capacitors are connected to the battery in parallel in J.

**Numeric** : A numeric value is expected and not an expression.

$U_p =$  \_\_\_\_\_

**Problem 3:** Suppose you have a 9.00 V battery, a  $2.6 \mu\text{F}$  capacitor, and a  $8.25 \mu\text{F}$  capacitor.

$$V_B = 9 \text{ V}$$

$$C_1 = 2.6 \mu\text{F}$$

$$C_2 = 8.25 \mu\text{F}$$



$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\frac{1}{C} = \frac{1}{2.6} + \frac{1}{8.25}$$

$$\frac{1}{C} = .384 + .121 = .505 = \frac{1}{C}$$

$$C = 1.97 \mu\text{F}$$

$$Q = CV$$

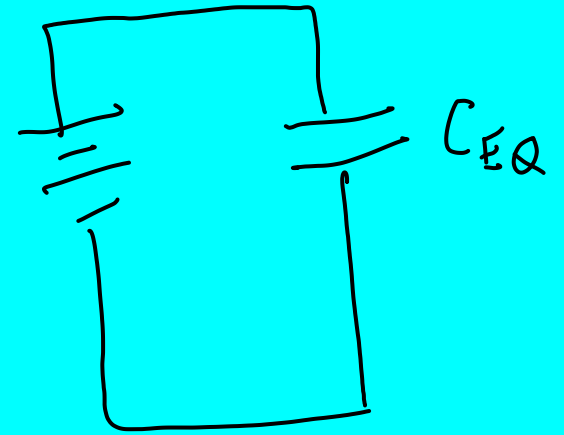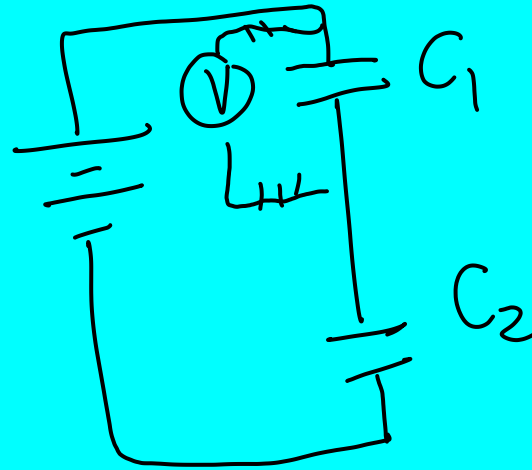

$$Q = C_{eq} V$$

$$(1.97 \times 10^{-6})(9)$$

$$Q \approx 18 \mu\text{C}$$

**Problem 3:** Suppose you have a 9.00 V battery, a 2.6  $\mu\text{F}$  capacitor, and a 8.25  $\mu\text{F}$  capacitor.

$$U = \frac{1}{2} QV = \frac{1}{2} CV^2$$

$$U = \left(\frac{1}{2}\right)(1.97 \mu\text{F})(9\text{V})^2$$


---

$$Q = \underline{CV}$$


$$Q = (10.85 \mu\text{F})(9)$$

$$Q = \underline{97.6 \mu\text{C}}$$

$$C_{eq} = C_1 + C_2 = 10.85 \mu\text{F}$$

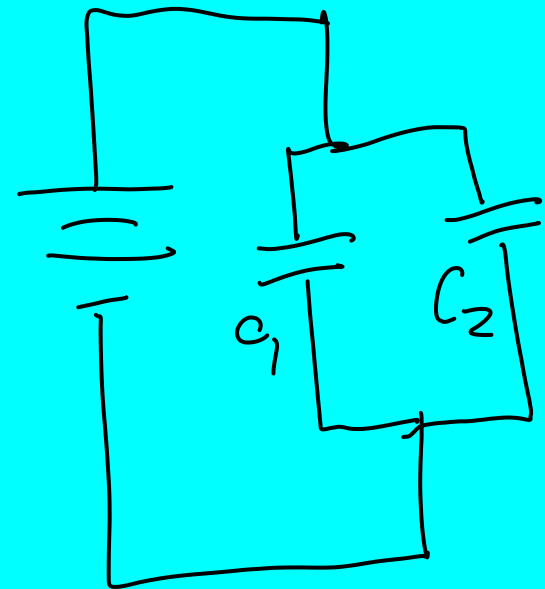

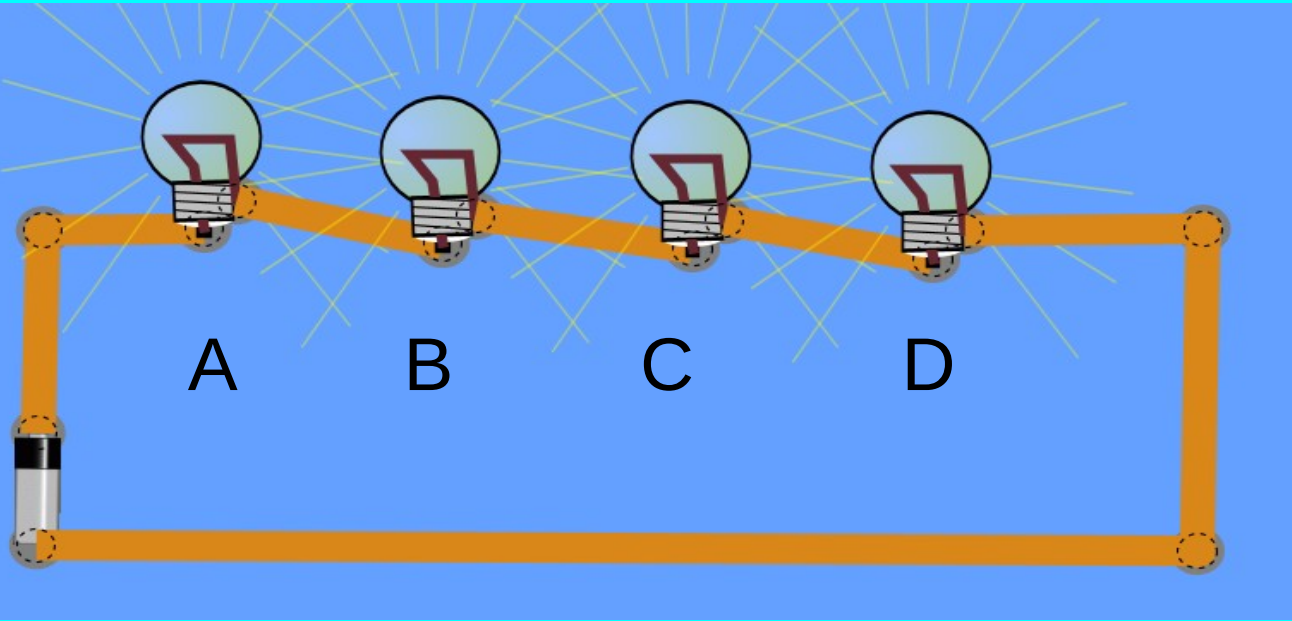**Problem 3:** Suppose you have a 9.00 V battery, a **2.6**  $\mu\text{F}$  capacitor, and a **8.25**  $\mu\text{F}$  capacitor.



Four light bulbs are in series as shown. Light bulb “C”  
Is removed. What happens?

- A. Bulbs “A” and “B” and “D” remain lit the same brightness
- B. Bulbs “A”, “B”, and “D” remain lit and get brighter
- C. Bulbs “A” and “B” get brighter, and bulb “D” goes out
- D. Bulbs “A” and “B” remain lit the same brightness,  
and bulb “D” goes out
- E. Bulbs “A”, “B” and “D” go out.

# Equivalent Resistors

If you replace resistors with an equivalent resistor then:

1) The current through the equivalent resistor is the same as the TOTAL current through the original circuit.

2) The power used by the equivalent resistor is the same as the TOTAL power used by the original circuit.

3) The sum of the power used at each original resistor equals the power used by the equivalent resistor.

4) The sum of the currents thru all parallel legs is the same as the current through the equivalent resistor.



# Equivalent Capacitors

If you replace capacitors with an equivalent capacitor then:

1) The charge on the equivalent capacitor is the same as the charge on any series capacitor in the original circuit.


2) The sum of the charges on all parallel legs is the same as the charge on the equivalent capacitor.

What is the equivalent resistance of this circuit?

What is the voltage across the 2-Ohm resistor?

What is the voltage across the 3-Ohm resistor?


$$V_B = 12 \text{ V}$$

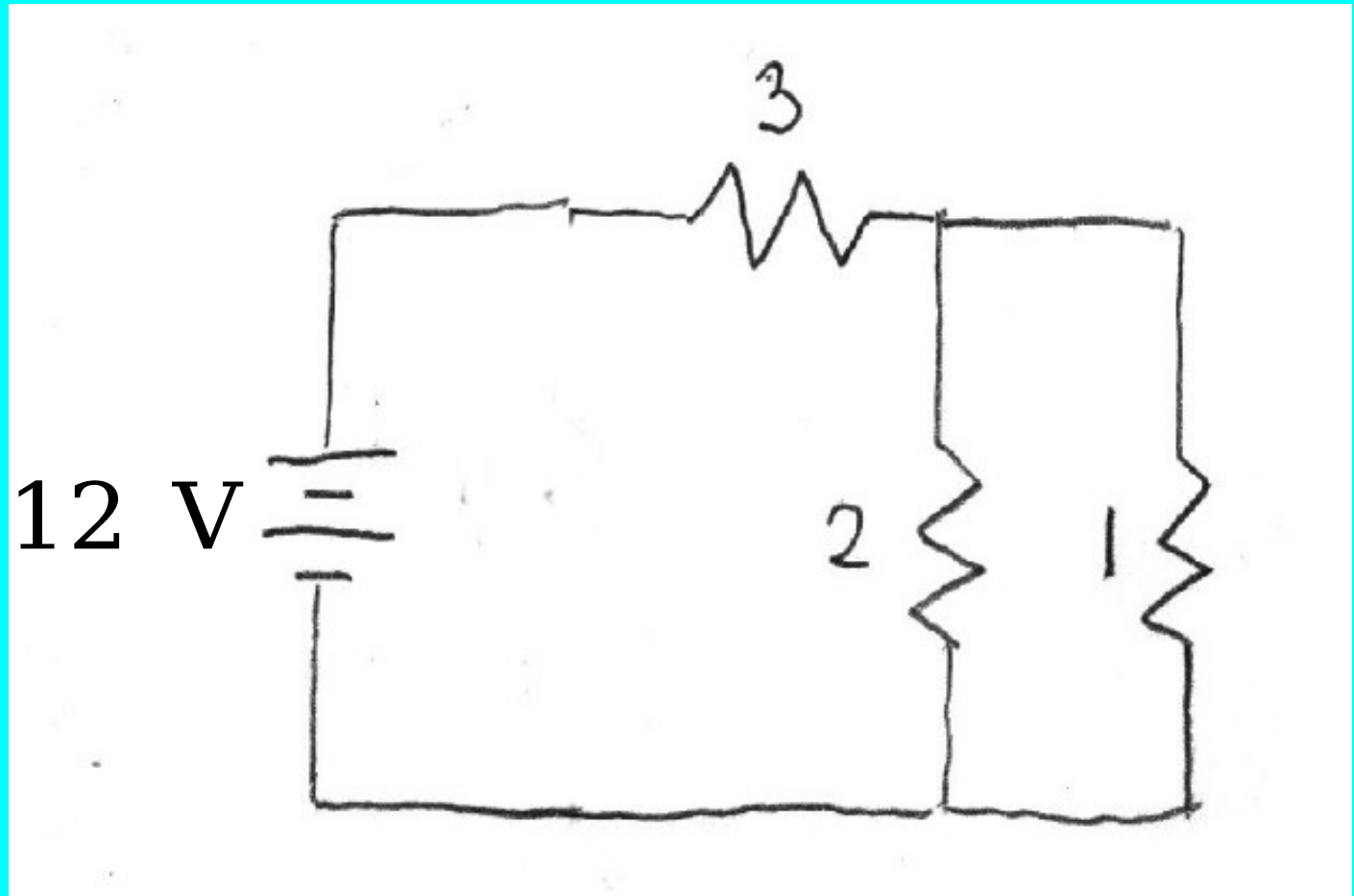

$$R_{\text{eq}} = ? \dots$$

$$\Delta V_2 = ? \dots$$

$$\Delta V_3 = ? \dots$$

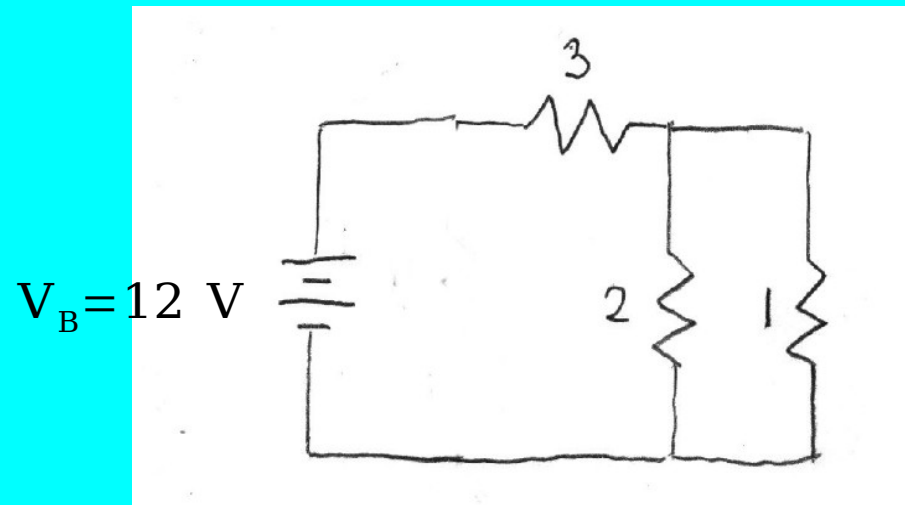

# Solving resistor network problems


- 1) Redraw the circuit as needed to see what parts are in series and what parts are in parallel.
- 2) Replace each section with an equivalent resistor for that section.
- 3) Combine equivalent resistors to get down to a single resistor. Get total current.
- 4) Apply current to all series sections to get voltage drop.
- 5) Apply voltage drop to all parallel sections to get current.

What is the equivalent resistance of this circuit?

What is the voltage across the 2-Ohm resistor?

What is the voltage across the 3-Ohm resistor?


$$V_B = 24 \text{ V}$$

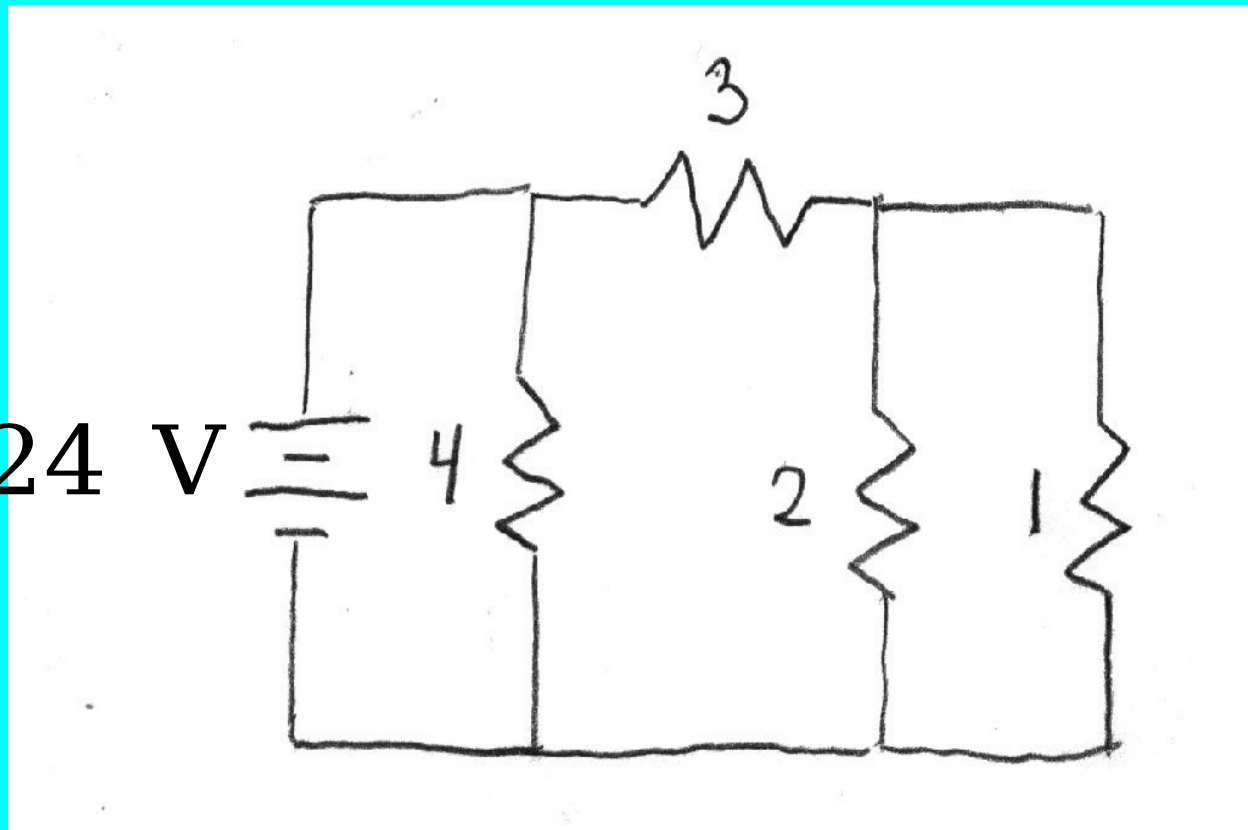

$$R_{\text{eq}} = ? \dots$$

$$\Delta V_2 = ? \dots$$


$$\Delta V_3 = ? \dots$$

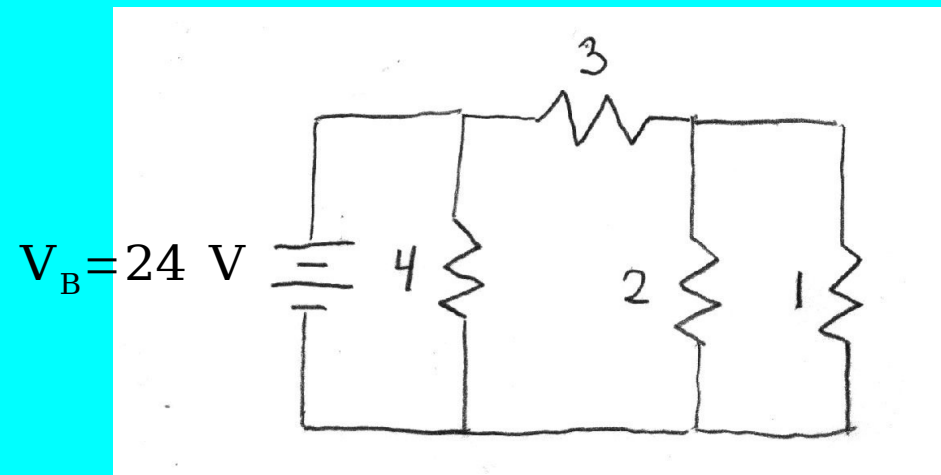

$$R_{\text{eq}} = ? \dots$$

$$\Delta V_2 = ? \dots$$

$$\Delta V_3 = ? \dots$$

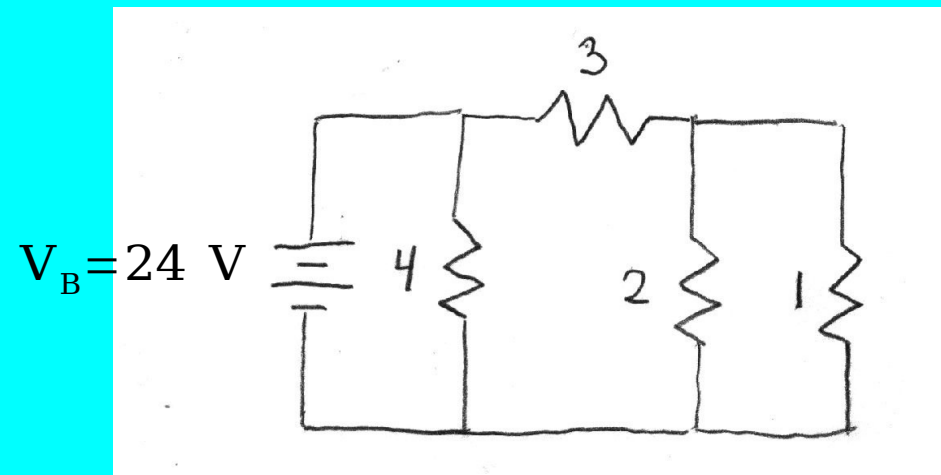

Redraw this circuit to show parallel/series combos better.  
Given  $V = 11$  Volts. Example of Kirchhoff's Voltage law.

$$I_4 = \frac{11}{4} \text{ A} \quad R_{\text{eqv}_{12}} = \frac{2}{3} \Omega \quad R_{\text{eqv}_{123}} = \frac{11}{3} \Omega$$

$$I_3 = 3 \text{ A}$$


$$I_1 = 2 \text{ A}$$

$$I_2 = 1 \text{ A}$$


$$V_3 = 9 \text{ V}$$

$$I_{\text{total}} = 5.75 \text{ A}$$

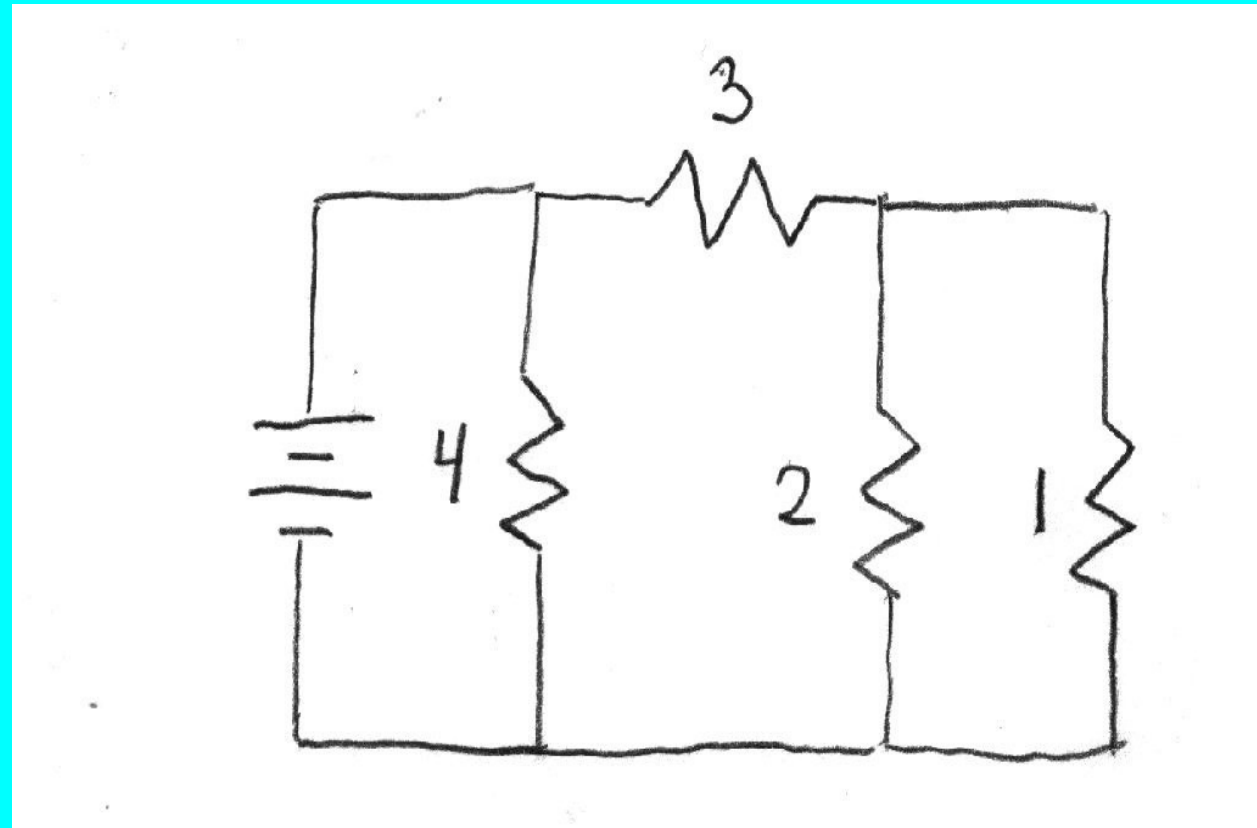
$$R_{\text{eqv}_{\text{total}}} = \frac{44}{23} \Omega$$





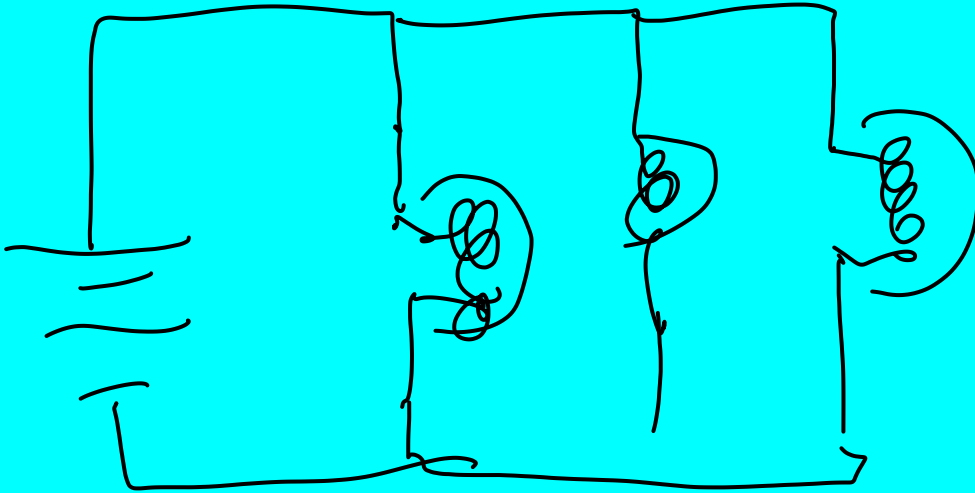



$$P = \frac{V^2}{R}$$

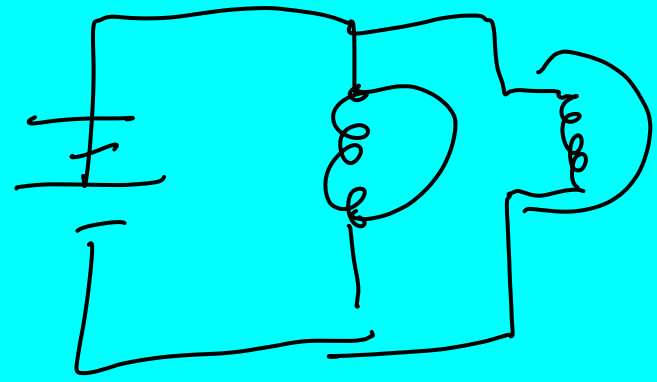



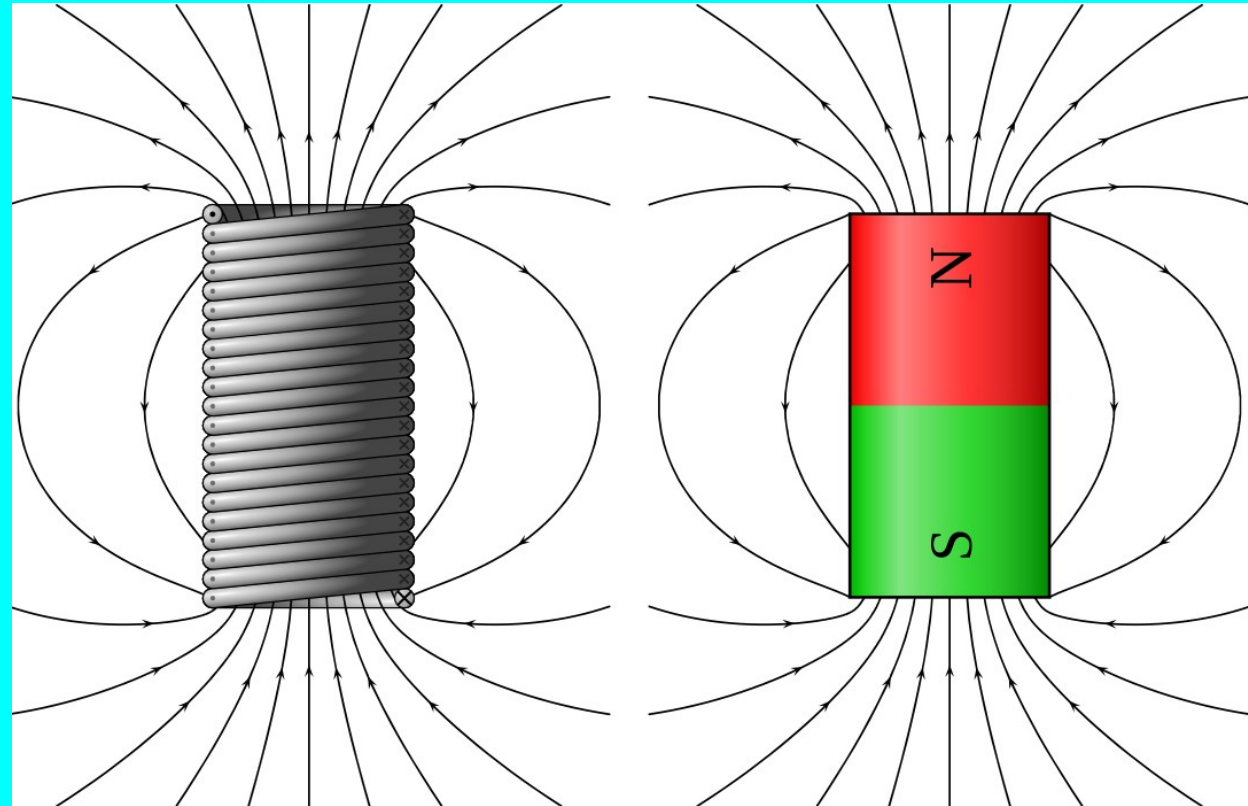
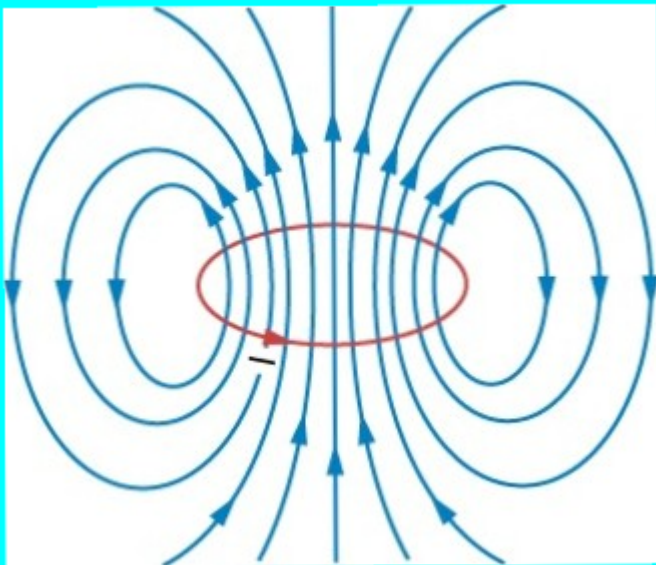
# Electromagnets

- A loop of wire is a basic electromagnet
- Many loops of wire (a coil or “solenoid”) is a better electromagnet.


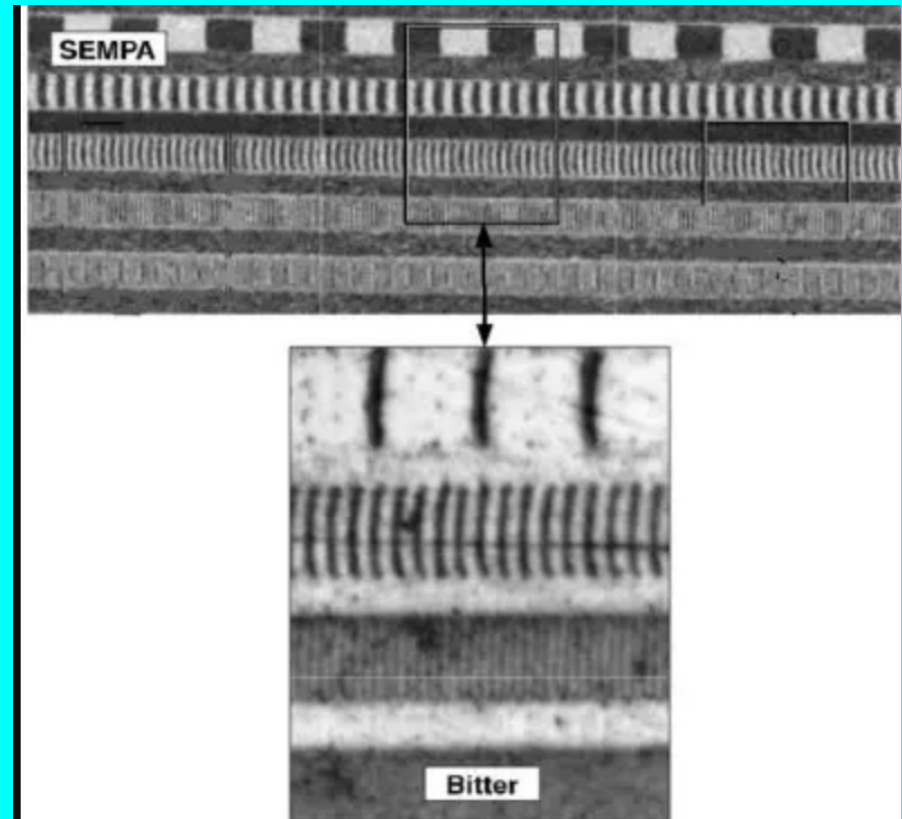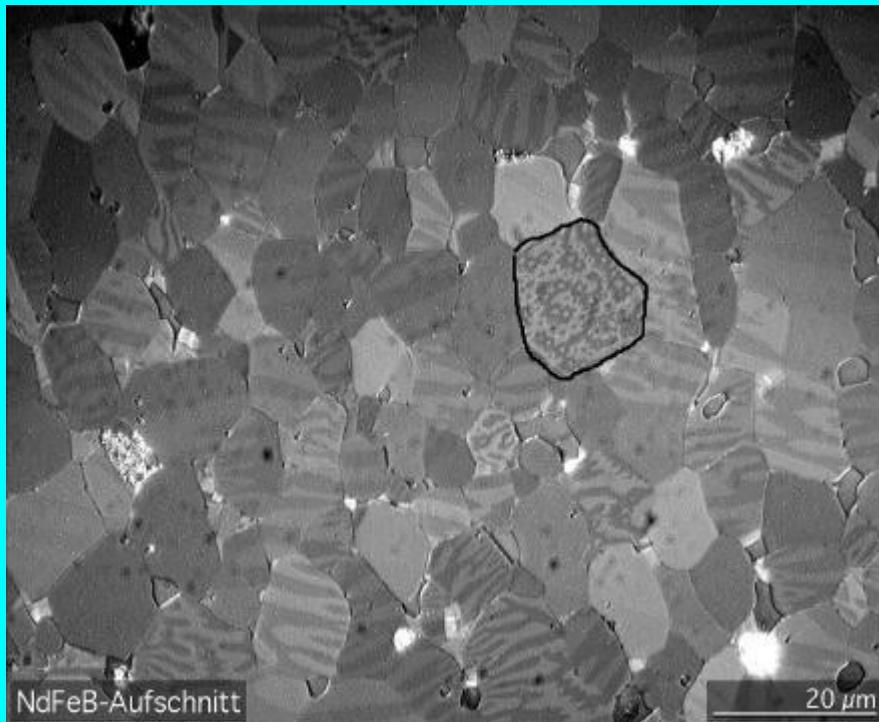
# Electromagnets and “Regular magnets”

- A loop of wire is a basic electromagnet
- Many loops of wire (a coil or “solenoid”) is a better electromagnet.
- Atoms with orbiting unpaired electrons are quantum electromagnets.
- They have magnetic “moments”
- Groups of atoms get together and make magnetic “domains”
- You “magnetize” iron by lining up its domains by exposing it to a strong magnet or by wrapping wire around it.



# Equations of Magnetism

$$\vec{F} = Q \vec{v} \times \vec{B} \quad \text{Force on charge } Q$$

$$\vec{F} = I \vec{L} \times \vec{B} \quad \text{Force on current } I$$


$$\vec{B} = \frac{\mu_0 I}{2\pi r} \hat{\phi} \quad \text{Field of Infinite wire}$$

$$\vec{B} = \frac{\mu_0 I}{2a} \hat{z} \quad \text{Field in center of wire loop}$$

$$\vec{B} = \mu_0 n I \hat{z} \quad \text{Field of an infinite coil (solenoid)}$$
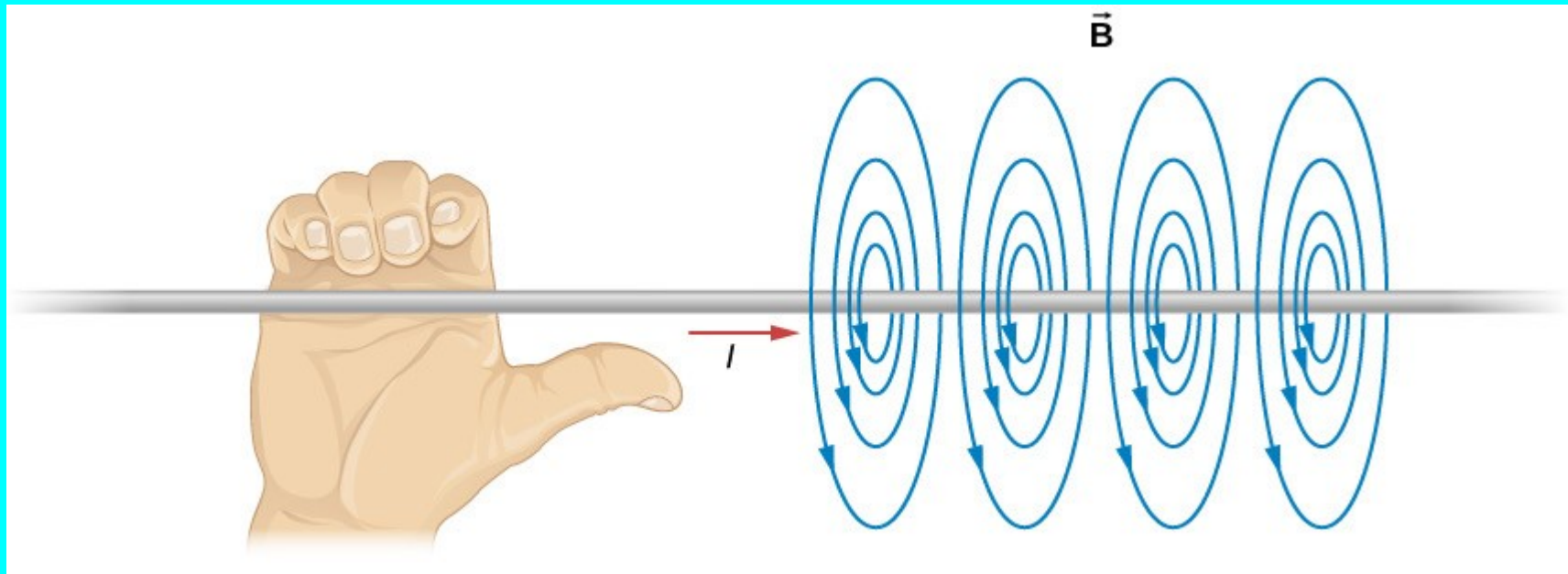
# Problem


- Two horizontal wires 3 meters long carry 15 Amperes directed to the right. They are separated by 1 cm.
- What is the magnetic field one cm above the bottom wire?
- What is the force on the top wire?



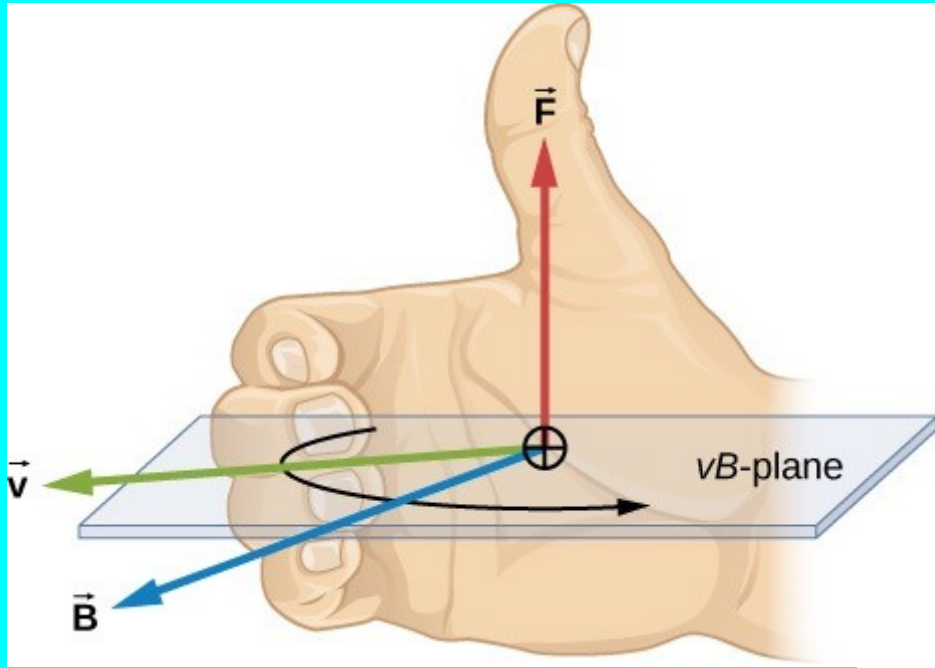
# Problem

- Two horizontal wires 3 meters long carry 15 Amperes directed to the right. They are separated by 1 cm.
- What is the magnetic field one cm above the bottom wire?





$$\vec{F} = I \vec{L} \times \vec{B}$$

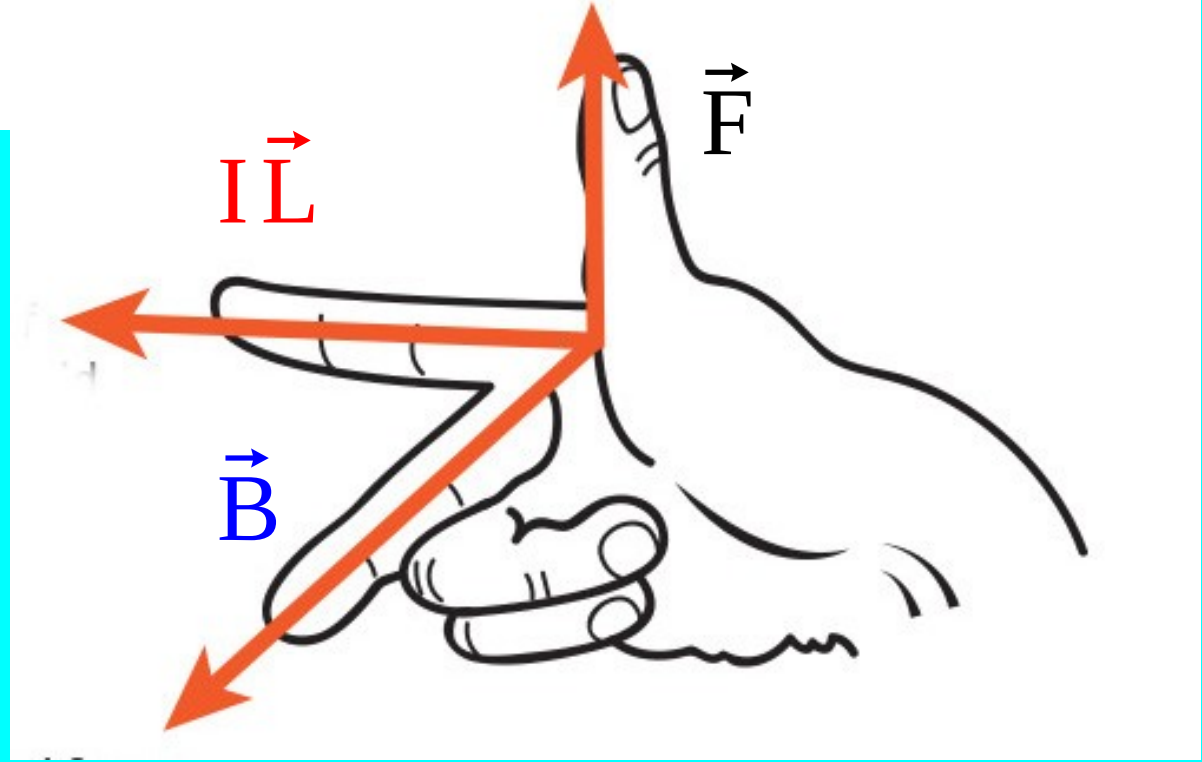


# Problem

- Two horizontal wires 3 meters long carry 15 Amperes directed to the right. They are separated by 1 cm.
- What is the force on the top wire?



# Next Week's Lab

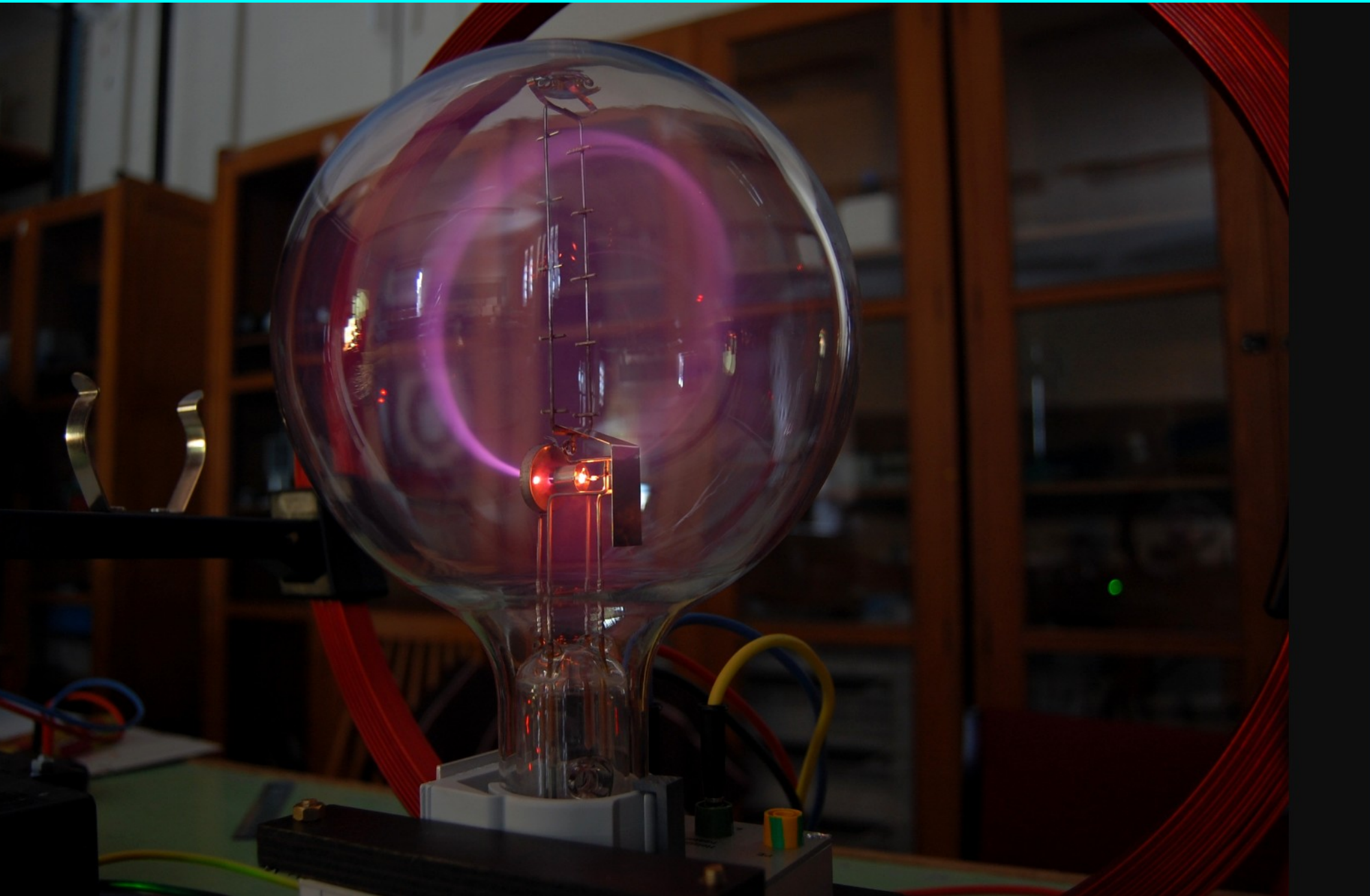

# Problem

- A uniform magnetic field of one milliTesla is in the z-direction
- An electron goes through a 1000 V potential drop.
- What path does the electron make in the field?
- What is the radius of the circle that it makes?





