
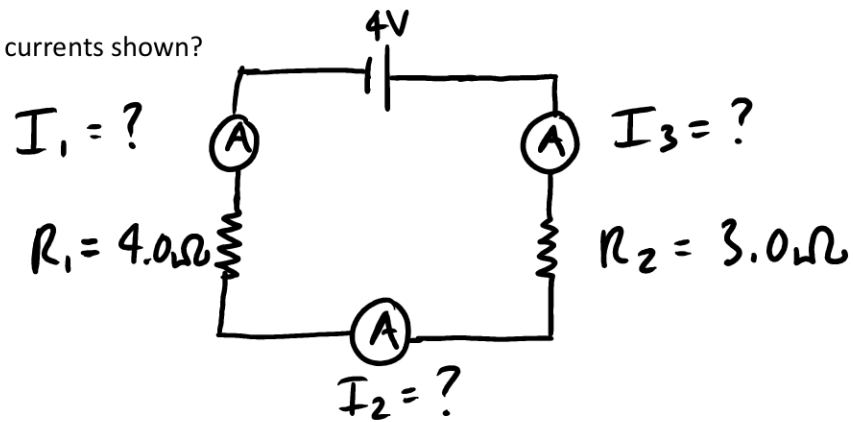


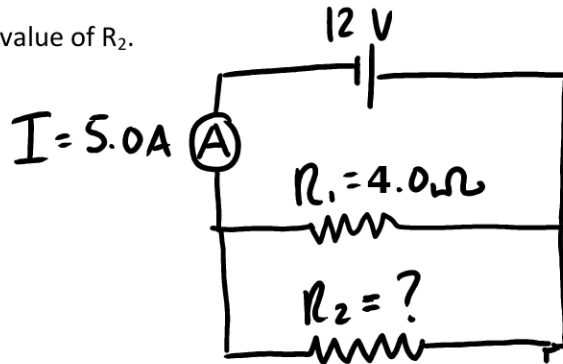
1) What are the values of the currents shown?




2) Find the value of R_2 .



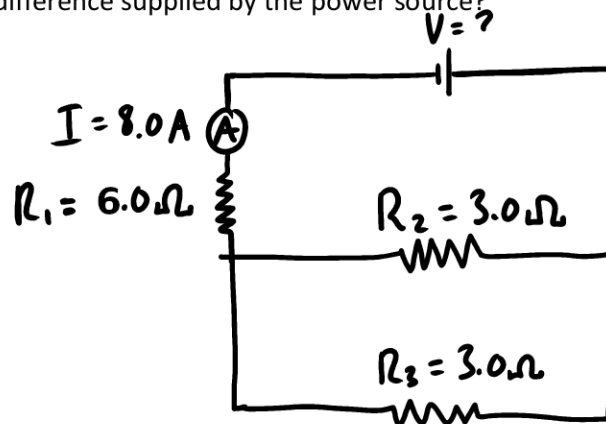
3) What is the potential difference supplied by the power source?



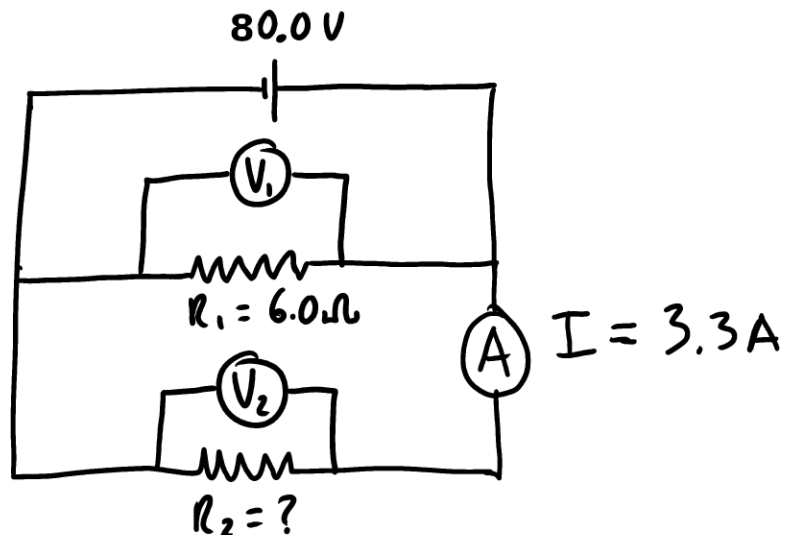
4) Find the values of V_1 , V_2 and R_2 .




5) Find the value of I_3 .

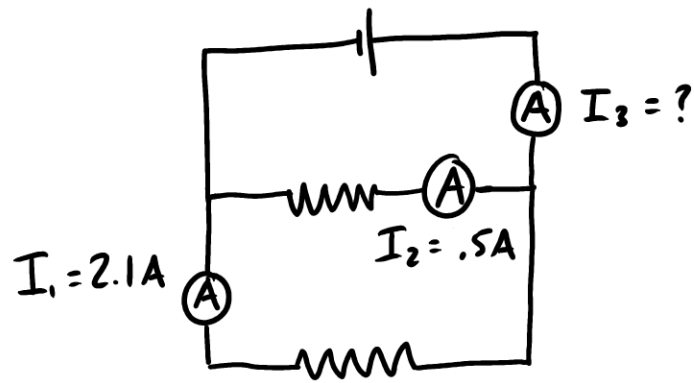


6) Find the value of V_2 .

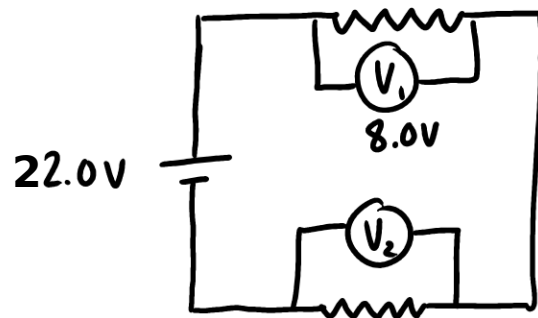


7) Find the value of V_2 and V_3 .

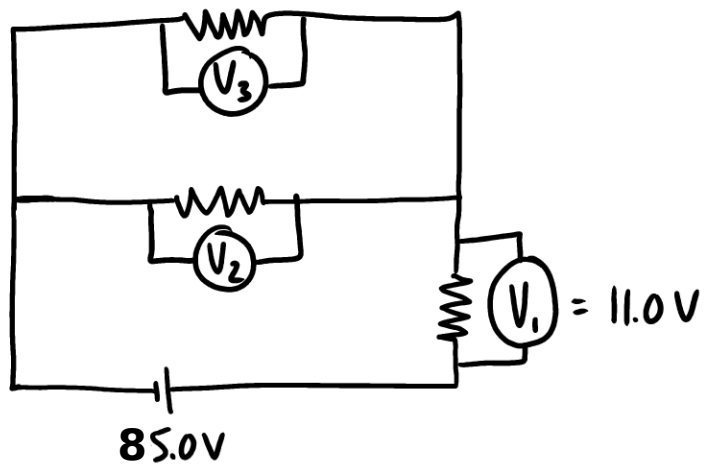

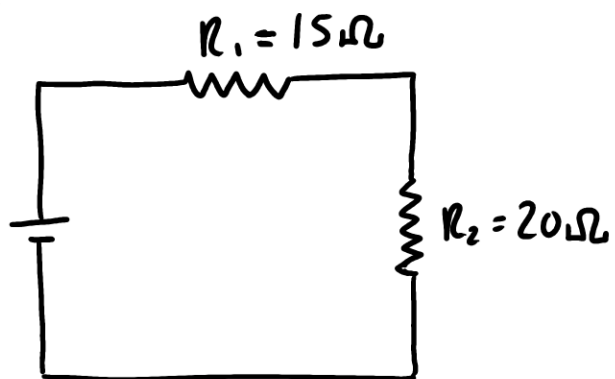
8) What is the total resistance in this circuit?



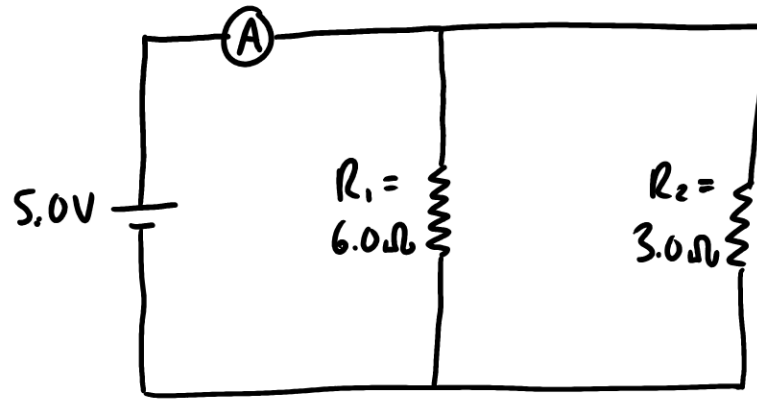13) What is the value of the total current in this circuit and the power dissipated by R_1 ?



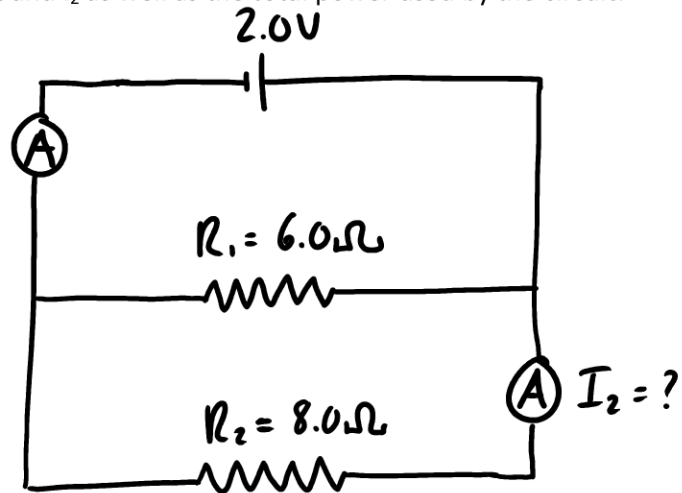14) Find the values of the total current and I_2 as well as the total power used by the circuit.



15) What are the values of I_1 , I_2 and I_3 ?

