

PHYSICS 570 – Master's of Science Teaching

“Electricity”

Lecture 13 – Equivalent Resistance

Instructor – Richard Sonnenfeld

mpsonnenfeld@gmail.com

575-835-6434

For Resistors in series

Voltages add across each resistor.

Current is the same everywhere in the circuit.

Equivalent resistance is sum of all resistances.

$$R_{\text{equivalent}} = R_1 + R_2 + R_3 + \dots$$

For Resistors in parallel

Voltage is the same across each resistor.

Current divides between resistors.

Equivalent resistance comes from following formula.

$$\frac{1}{R_{\text{equivalent}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Examples

Given a 3, 4 and 5 Ohm resistor in series and a 6 V battery.

What is equivalent resistance?

What is current?

What is power consumed by resistors?

$$R_{\text{equivalent}} = R_1 + R_2 + R_3 + \dots$$

Examples

Given a 3, 4 and 5 Ohm resistor in series and a 6 V battery.

$R_{eq} =$

$I =$

$P =$

Examples

Given a 10 Ohm a 20 Ohm and a 40 Ohm resistor in parallel and a 6 V battery.

What is equivalent resistance?

What is total current?

What is power consumed by each resistor?

What is total power consumed?

$$\frac{1}{R_{\text{equivalent}}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

Examples

Given a 10 Ohm a 20 Ohm and a 40 Ohm resistor in parallel and a 6 V battery.

R_{eq}

I_{total}

P_{total}

Homework is Lab 13

You will build one resistor in series with two resistors in parallel. The theory and experiment match beautifully!

$$R = \rho \frac{L}{A}$$