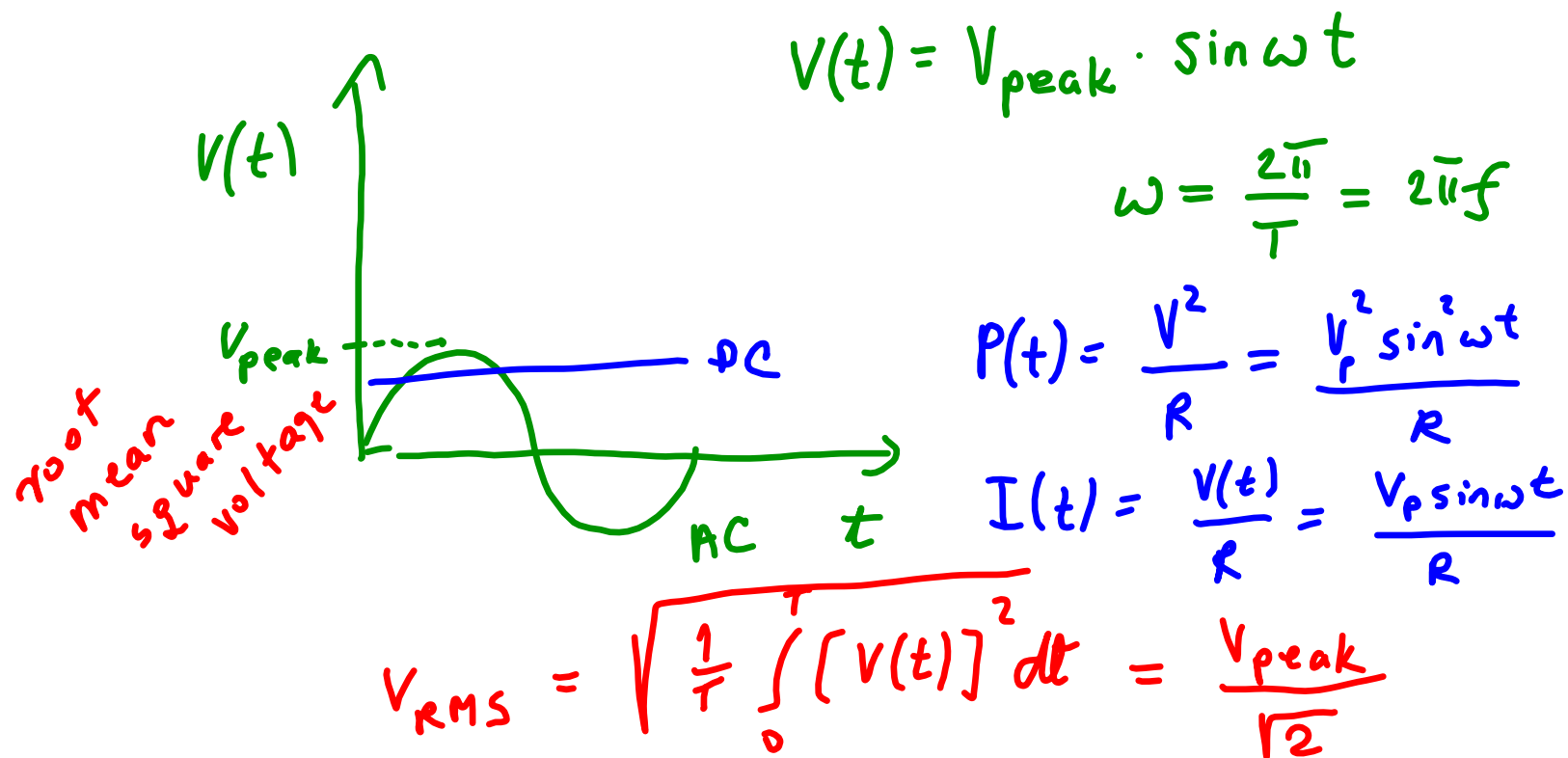


# AC / DC



$$V(t) = V_{peak} \cdot \sin \omega t$$

$$\omega = \frac{2\pi}{T} = 2\pi f$$

$$P(t) = \frac{V^2}{R} = \frac{V_p^2 \sin^2 \omega t}{R}$$

$$I(t) = \frac{V(t)}{R} = \frac{V_p \sin \omega t}{R}$$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T [V(t)]^2 dt} = \frac{V_{peak}}{\sqrt{2}}$$

$$V_{RMS} = \frac{V_{peak}}{\sqrt{2}} \quad \text{US}$$

$$V_{RMS} = 120 \text{ V}$$




$$170 \text{ V} = V_{peak}$$
$$f = 60 \text{ Hz}$$

$$\text{EU} \quad V_{RMS} = 220 \text{ V}$$
$$f = 50 \text{ Hz}$$

# Basic circuit

- single resistor & battery

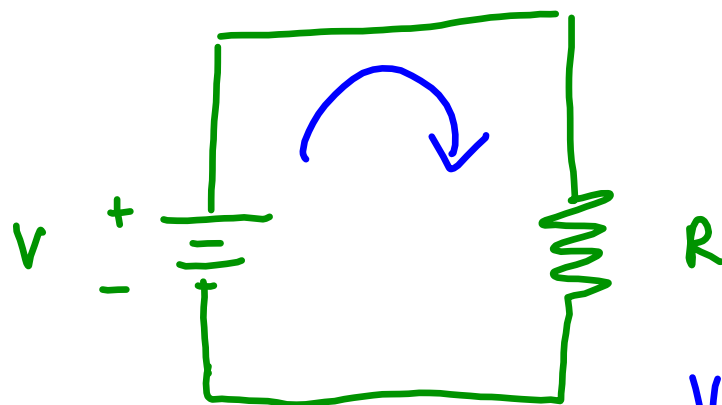

$$V = 20 \text{ V}$$

$$R = 10 \Omega$$


$$I = ?$$

$$V - V_R = 0$$

Ohm's law  $V_R = IR$

$$V - IR = 0$$

$$I = \frac{V}{R} = 2 \text{ A}$$

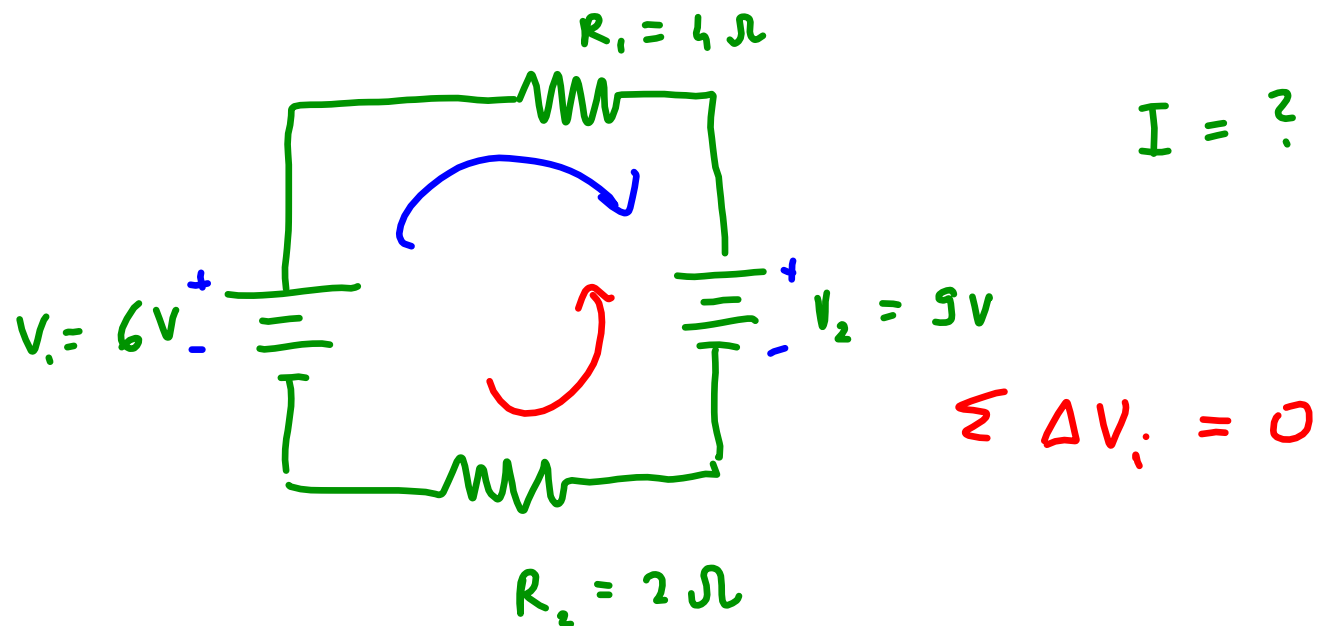


$$V_1 - IR_1 - V_2 - IR_2 = 0 \quad I = -0.5A$$

$$V_2 - IR_1 - V_1 - IR_2 = 0 \quad I = +0.5A$$
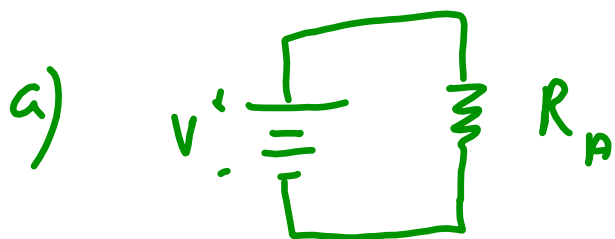
## Resistors in series

3 light bulb that are identical


note  
I is the same as there are no junctions



$$V - IR_A = 0$$

$$V = IR_A$$

$$R_A = R_B + R_C$$

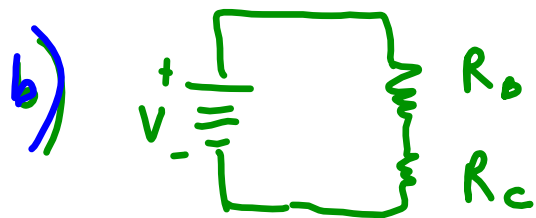

$$V - IR_B - IR_C = 0$$


$$V = I(R_B + R_C) = 0$$

A battery is a source of  $V$ , it provides  $I$  but the amount of it depends on resistance of the load

Ammeters - devices that measure the current

(A) - must be placed in series with a device that it measures

## Parallel resistors

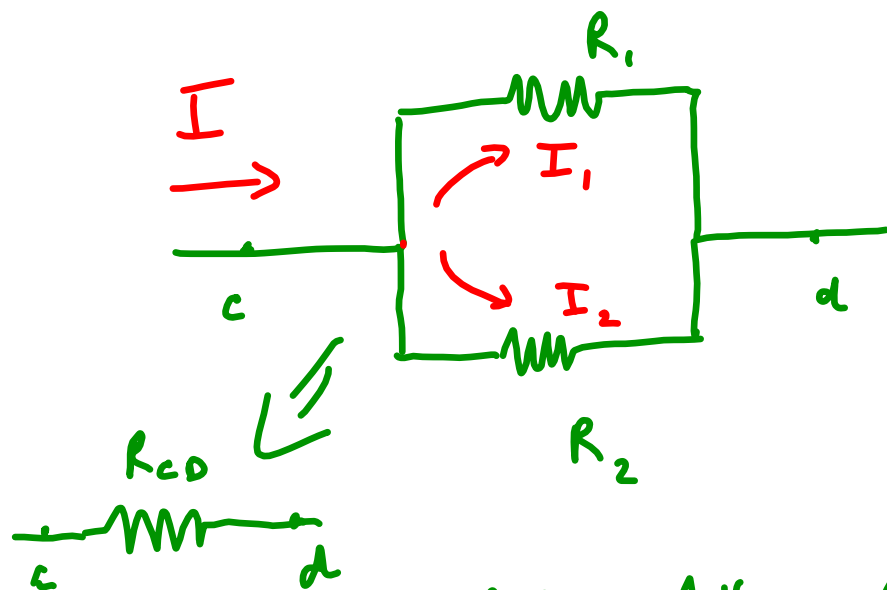

$$I = I_1 + I_2$$

$$I = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2}$$

$$I = \frac{\Delta V_{cd}}{R_{cd}}$$

$$\Delta V_1 = \Delta V_2 = \Delta V_{cd}$$

$$\frac{1}{R_{cd}} = \frac{1}{R_1} + \frac{1}{R_2}$$

In series  $R_{eq} = R_1 + R_2 + R_3 + \dots$

In parallel  $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_2} + \dots$

Ex



