

$$J = \frac{E}{\rho} \quad \textcircled{*} I = \frac{V}{R}$$


$$I = J \cdot A \quad A \text{ surface area}$$

$$I = \frac{E}{\rho} \cdot A$$

$$\textcircled{*} R = \left(\rho \right) \frac{L}{A}$$

$$\rho = \frac{RA}{L}$$
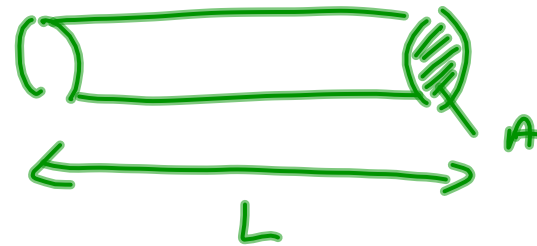
$$I = \frac{E \cdot L}{RA} \cdot A = \frac{E \cdot L}{R} = \frac{V}{R}$$



Example of R (light bulb)

R resistance [Ω] Ohm

$$I = \frac{V}{R} \quad \text{or} \quad V = I \cdot R \quad \text{or} \quad R = \frac{V}{I} \quad \text{Ohm's law}$$

Electric power

$$P = I \cdot V = I \cdot I \cdot R = \frac{V^2}{R} \\ = I^2 R \quad [W]$$


Conservation of current / charge

$$\bar{I} = \frac{\Delta Q}{\Delta t}$$



conservation of mass


$$\text{flow}_{in} = \text{flow}_{out}$$

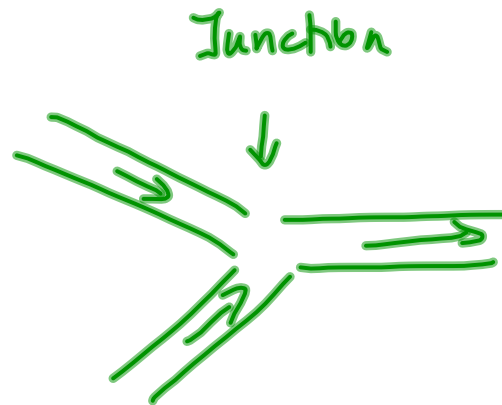

$$\sum I_{in} = \sum I_{out}$$

Kirchhoff's
junction law

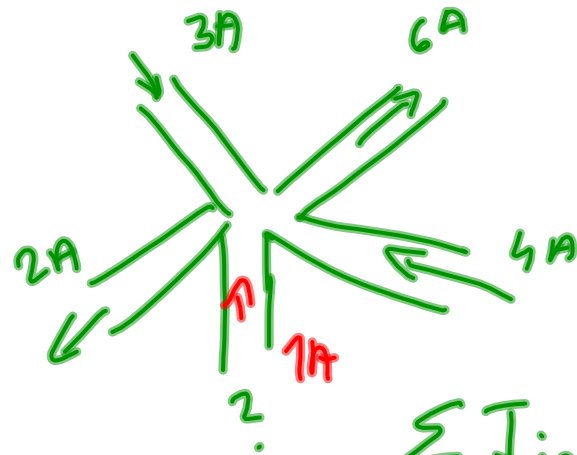The sum of the currents into a junction must equal to the sum of the currents leaving the junction. (Cons. of current / charge)



$$\sum I_{in} = 7A$$

$$\sum I_{out} = 8A$$

A point where a wire branches is called a junction.

2 ways to decrease current - decrease the amount of charge
- decrease the speed (v_d)

$$I = \frac{\Delta Q}{\Delta t}$$


Resistors don't change current, but use energy.

Kirchhoff's loop law

The sum of all the potential differences encountered while moving around a loop or closed path is zero.

$$\Delta V_{\text{loop}} = \sum_i (\Delta V)_i = 0$$


conservation
of energy

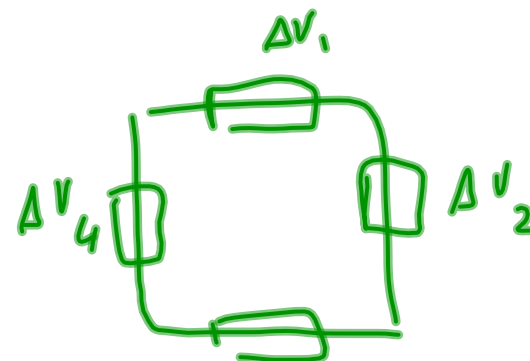

$$\Delta V_1 + \Delta V_2 + \Delta V_3 + \Delta V_4 = 0$$

Circuit elements


Battery

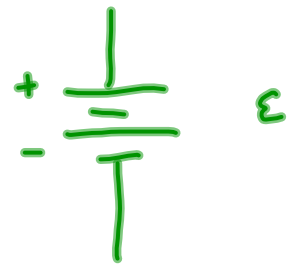

Resistor



Wire

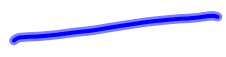


Junction




Switch


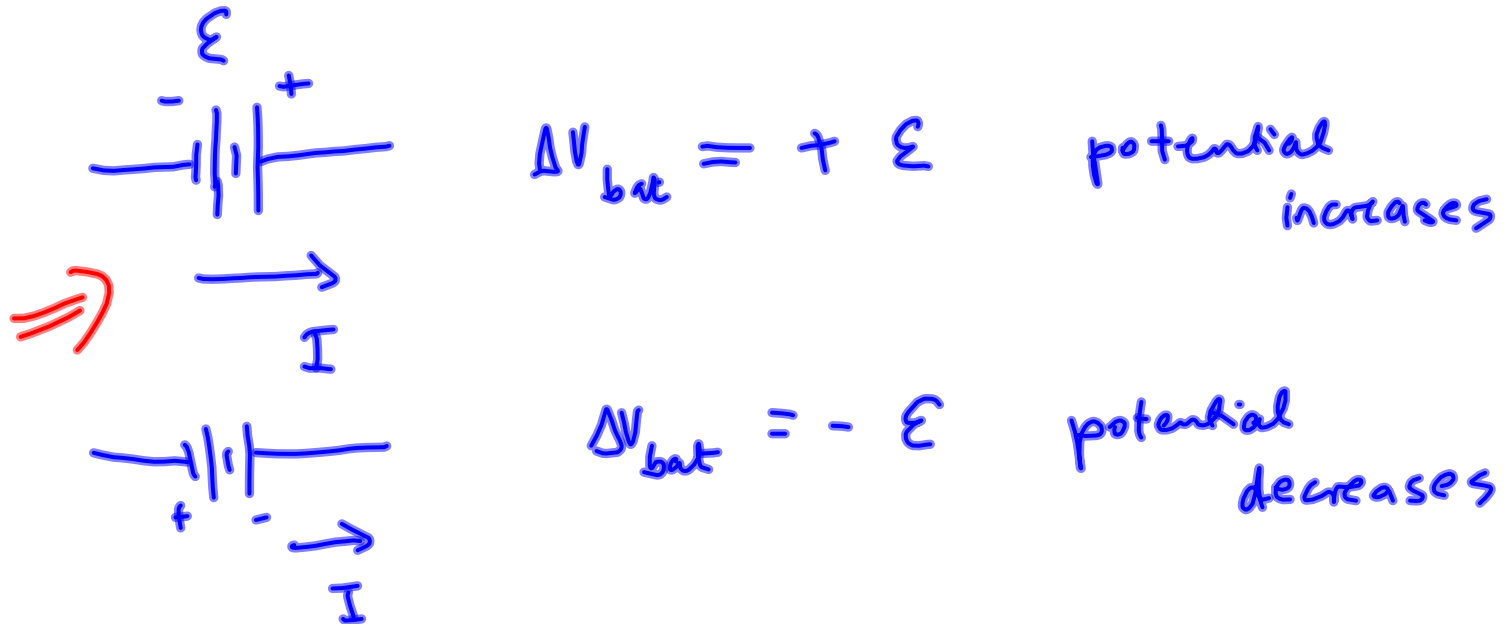
$$\Delta V = V_{\text{downstream}} - V_{\text{upstream}}$$


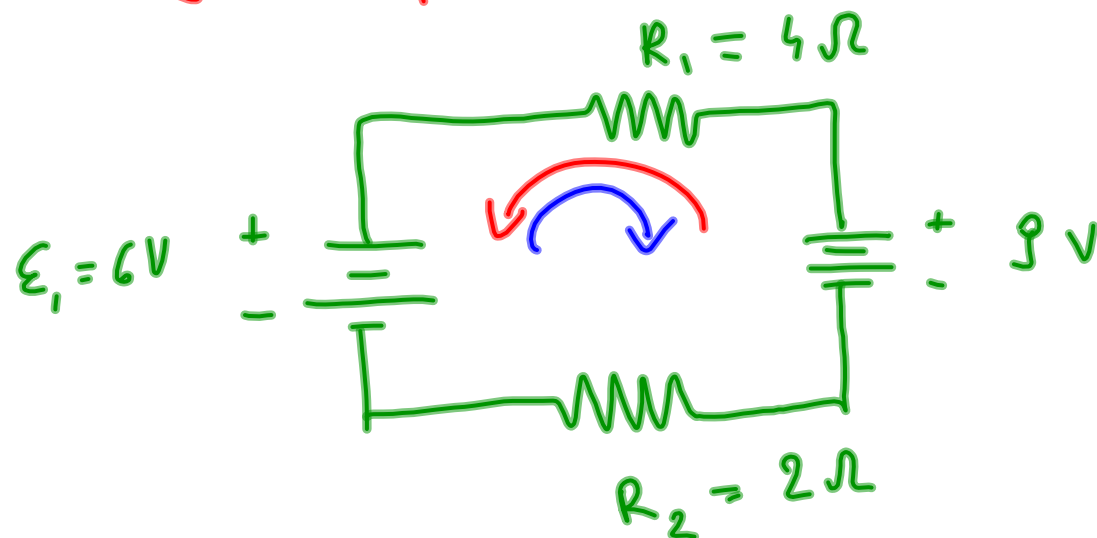
$$9V - IR_1 - 6V - IR_2 = 0 \quad I = 0.5A$$



Find the
current &
potential across
each resistor.

Remember $V = I \cdot R$

$$\Sigma(\Delta V)_s = 0$$

$$6V - IR_1 - 9V - IR_2 = 0$$


$$-3V = I(6\Omega) \Rightarrow \boxed{I = -0.5A}$$

$$\Delta V_1 = -IR_1 = -2V$$

$$\Delta V_2 = -IR_2 = -1V$$

Resistors in series & parallel

in series

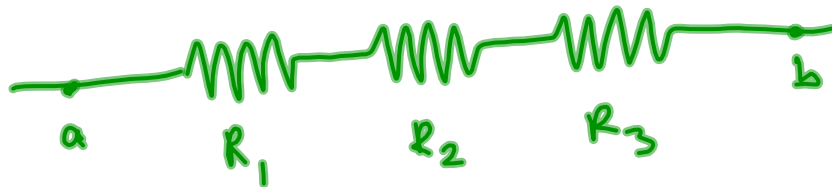

- no junctions
- I is the same

$$\begin{aligned}\Delta V_{ab} &= \Delta V_1 + \Delta V_2 + \Delta V_3 \\ &= IR_1 + IR_2 + IR_3 \\ &= I(R_1 + R_2 + R_3)\end{aligned}$$


$$R_{eq} = R_1 + R_2 + R_3 + \dots \quad \text{in series}$$

Ammeters - device that measures the current in a circuit

- (A)

- must be placed in series with a device that it measures

Parallel resistors

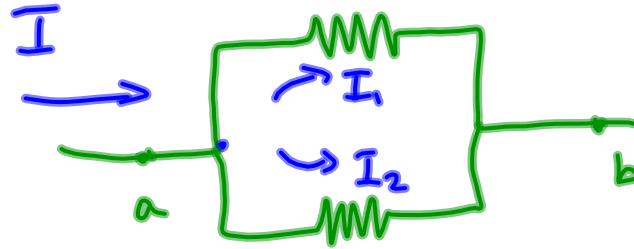

the same potential
difference

junction !

$$I = I_1 + I_2$$

$$\Delta V_{ab} = \Delta V_1 = \Delta V_2$$

$$I = \frac{\Delta V_1}{R_1} + \frac{\Delta V_2}{R_2}$$

$$= \Delta V_{ab} \left(\frac{1}{R_1} + \frac{1}{R_2} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

Voltmeter -
in parallel



ΔV , I
through
each
resistor?

$$I = \frac{V}{R}$$

$$I = \sum I$$

$$I_1 = \frac{9}{15} A$$

$$I_2 = \frac{9}{4} A$$

$$I_3 = \frac{9}{8} A$$

$$I = \frac{9}{15} + \frac{9}{4} + \frac{9}{8}$$

$$= 4A$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I = \frac{V}{R_{eq}}$$